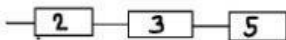
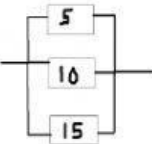
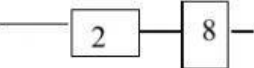
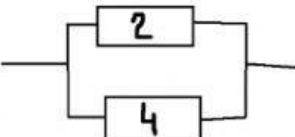


Задание 1

Сопротивление		A		Вт
Напряжение		U		Ом
Сила тока		R		В
Электрический заряд		I		Кл
		q		А

Задание 2

			
$R_{общ} =$	$R_{общ} =$	$R_{общ} =$	$R_{общ} =$
$U_{общ} = 20 \text{ В}$	$U_{общ} = 20 \text{ В}$	$U_{общ} = 20 \text{ В}$	$U_{общ} = 20 \text{ В}$
$I_{общ} =$	$I_{общ} =$	$I_{общ} =$	$U (2\text{ом}) =$
$I(3\text{ом}) =$	$I(5\text{ ом}) =$	$I(2\text{ ом}) =$	$I (4\text{ом}) =$
$U (2\text{ом}) =$	$U (2\text{ом}) =$	$U (8\text{ ом}) =$	