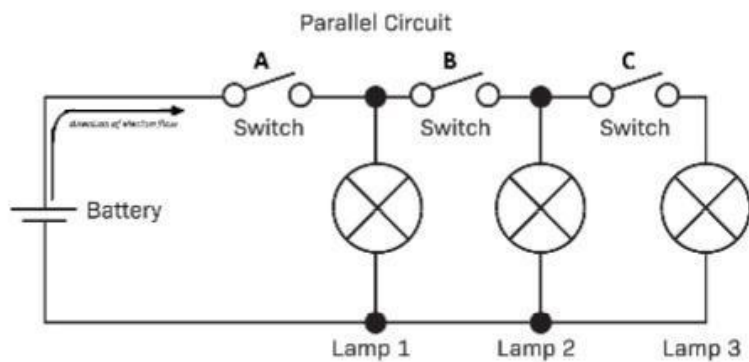




If just Lamp 1 is going to be on which switches should be closed, and which should be opened.

Switch A Open Closed

Switch B Open Closed

Switch C Open Closed