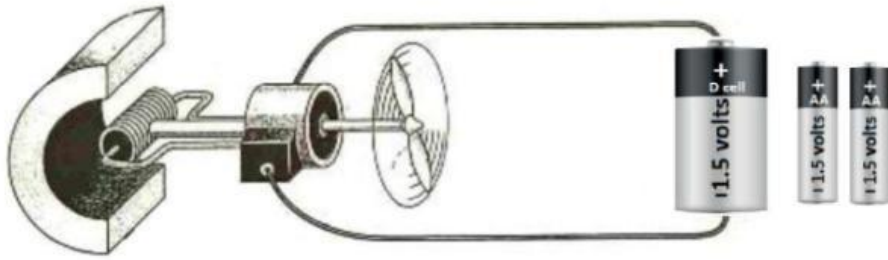


QUESTION 5



If the motor circuit pictured above was modified so that the single "D cell" battery was replaced with 2 "AA batteries" the speed of the fan rotation would (increase, decrease, remain the same)