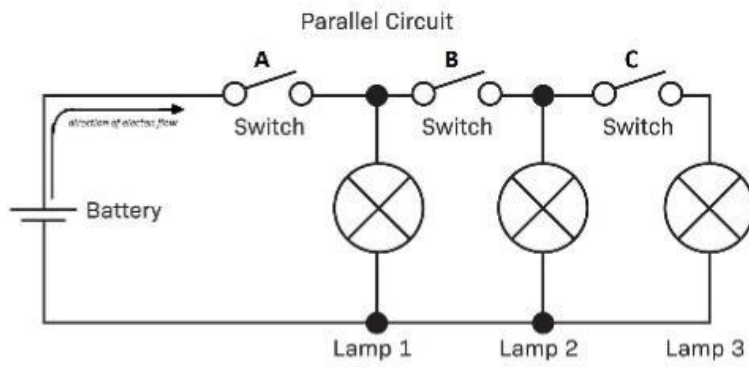




In order for just Lamp 3 to be off which switches should be opened and which should be closed?

Switch A Open Closed

Switch B Open Closed

Switch C Open Closed