

series

parallel

not light

series

will still work

1. Electrical components can be connected in 1 or in parallel

2. In a 2 circuit there is only one route for the current to flow around the circuit

3. In a series circuit if one bulb stops working, the other bulb will 3

4. In a 4 circuit there is more than one route for the current to flow around the circuit

5. In a parallel circuit if one bulb stops working, the other bulb 5