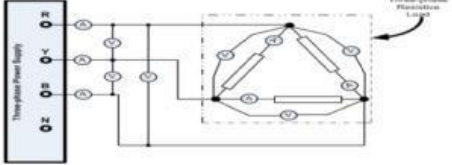
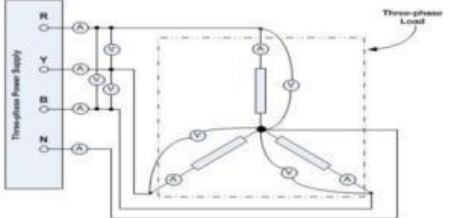




مقرر ماك805 قسم الكهرباء - دعم فئات الطلاب

Matching –Match the sentences to suit them in the table.

No	Column A	Column B
1-	Formula of power	$I_N = 0$ $R_{ph1} = R_{ph2} = R_{ph3}$
2-	Star Connection	$P = \sqrt{3} \times V_L \times I_L \times P.F$ $P = \sqrt{3} \times V_{PH} \times I_{PH} \times P.F$
3-	(AT BALANCE LOAD)	
4-	(AT UNBALANCE LOAD)	to supply and ends connected together.
5-	Delta Connection	
6-	in delta connection Start connect	$I_N \neq 0$ $R_{ph1} \neq R_{ph2} \neq R_{ph3}$
7-	in star connection Starts(begins) connect	To the end in delta connection

Teacher: - AHMED SHAHIN

HEAD OF SECTION: -Reda Hadi

HEAD MASTER: SAYED REDA