


Zaporedna vezava porabnikov

1. Rezultate, ki si jih dobil pri merjenju toka z virtualnim laboratorijem, vnesi v tabele.




a) Vezava ene žarnice.

U (V)	I (A)
9 V	

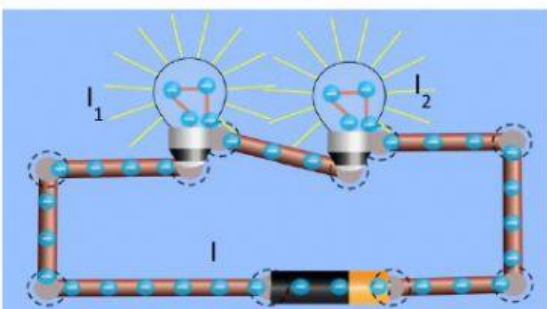

b) Zaporedna vezava dveh žarnic.


U (V)	I (A)	I ₁ (A)	I ₂ (A)
9 V			

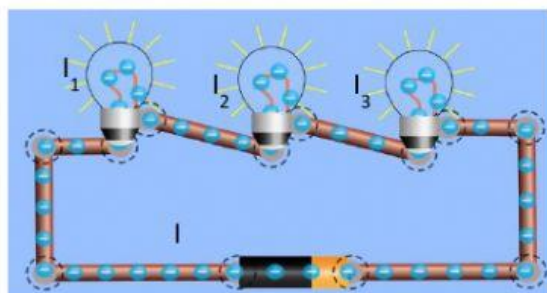

c) Zaporedna vezava treh žarnic.


U (V)	I (A)	I ₁ (A)	I ₂ (A)	I ₃ (A)
9 V				

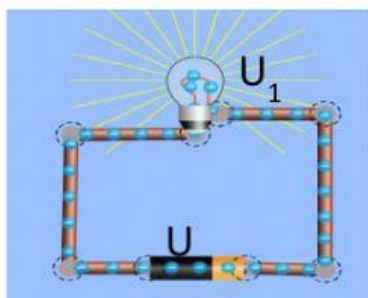2. Rezultate, ki si jih dobil pri merjenju napetosti z virtualnim laboratorijem, vnesi v tabele.




a) Vezava ene žarnice.

U (V)	U ₁ (V)

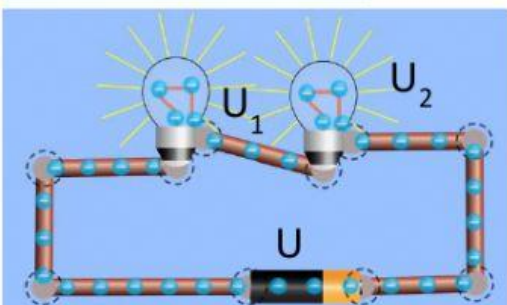

b) Zaporedna vezava dveh žarnic.

U (V)	U ₁ (V)	U ₂ (V)

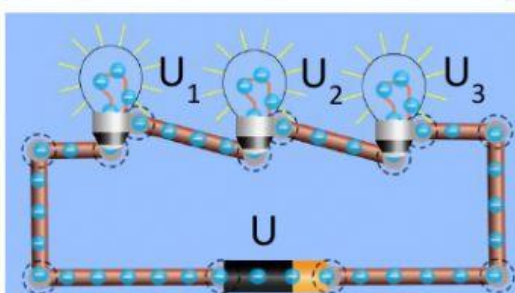

c) Zaporedna vezava treh žarnic.

U (V)	U ₁ (V)	U ₂ (V)	U ₃ (V)