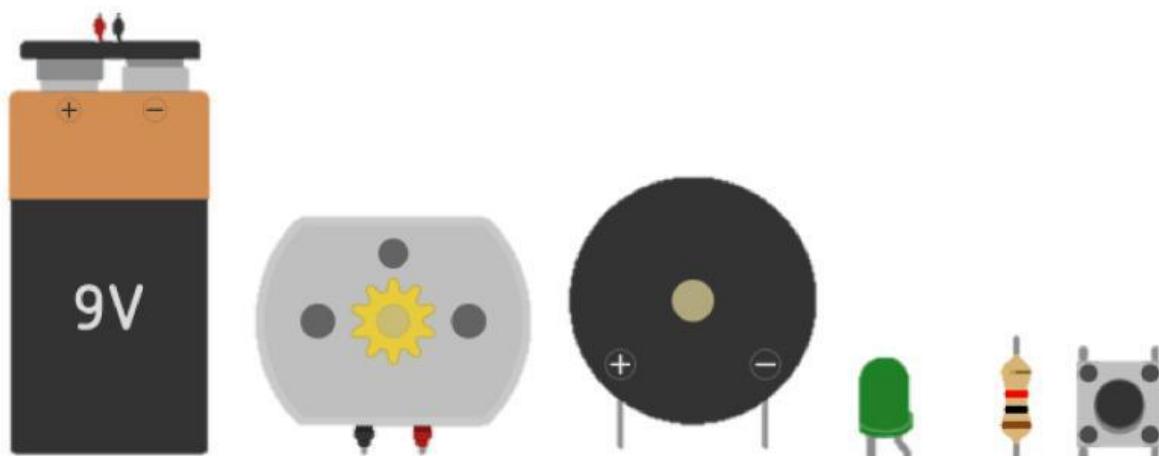




Name:

1- Connect every electrical component with its name:



LED

Buzzer

Resistor

Voltage
Source

Push
button

Motor

2- Connect every electrical concept with its meaning:

Voltage

The flow of electricity through an electrical conductor

Electric Current

A measure of the opposition to the flow of current in an electrical circuit.

Resistance

The “pressure” that pushes electricity through a conducting loop

3- Determine which circuit will produce light by the LED:

