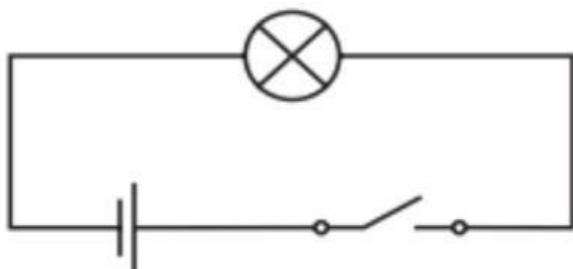


Label the components of the following circuit diagrams. Also mention the terminals of the battery.

Case 1: The \_\_\_\_\_ will \_\_\_\_\_ glow because the \_\_\_\_\_ is open.



Case 2: The \_\_\_\_\_ will glow because the switch is \_\_\_\_\_.

