









Name: _____
Class: 2A, 2B

Simple Circuit
Science Worksheet#7

---/--/2026
10 Marks

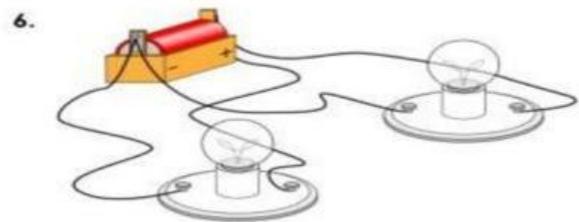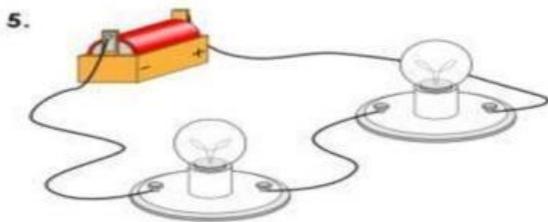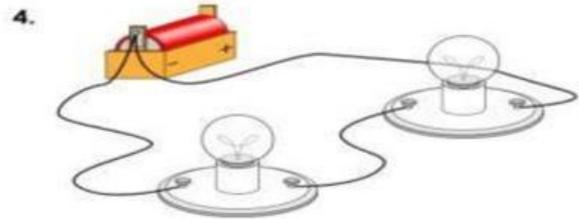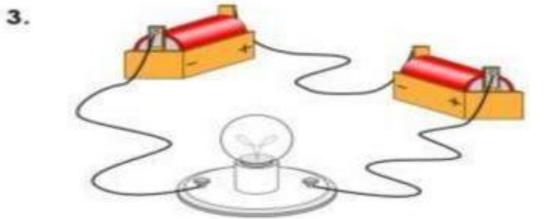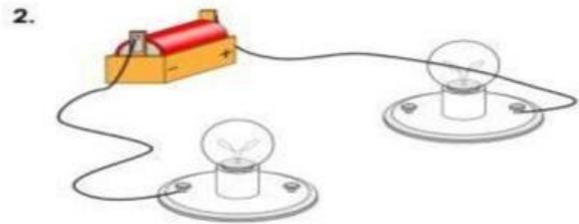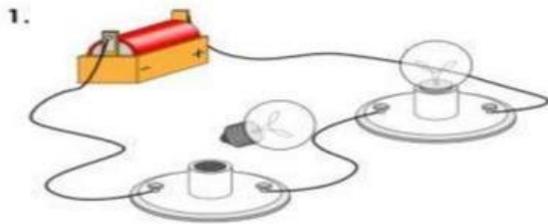1. Write Will light or Will not light based on the circuit: /10





Will light

or

Will not light

