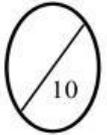


Name:		ID		Class:		Date:	
-------	--	----	--	--------	--	-------	--

**ELEC 808**  
**Class work 3- Converting Boolean expression to logic circuit and truth table**



**Q: Convert the following Boolean expressions to logic circuit diagrams & extract the truth table.**

**Construct the circuit on a breadboard.**



**a)  $Y = (A + B)C$**

**1 Mark/column**

**3 Marks**

**Drawing area:**

C	B	A		
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

**Checklist**

Sl.No	Task	Max marks	Mark obtained
1	Assembly on bread board correctly.	2.5	
2	Operation matching truth table.	2.5	
3	Followed safety rules.	Yes / No	
4	<b>Total mark</b>	<b>5</b>	