

Name:

Grade: 4th Section:

Date: / / 2026



Al Ridwan Schools
Inspiring schools

Subject:Science.....

Term:Second.....

Duration:

Worksheet (2)

Making circuits

Apply

Q1: Write the words from the box in its correct place:

Mobile phones / Current / Battery / Buzzer / Pull cord / Circuit / Lights at homes / Motor Button/ Complete

1. We use the word ----- to describe a group of cells connected together.
2. ----- and ----- are components that we can add to circuits.
3. Two types of switches are ----- and -----
4. When electricity moves around the circuit, this is called an electric -----
5. A ----- is a complete path through which electricity flows.
6. Two uses of electricity are ----- and -----

Q2: Write the way of connecting a wire to a component in its correct place:

Plug / Bare wires / crocodile clip

Knowledge







Q3: What happens to the circuit when:

Analyze

a. The switch is ON: 1. -----

2. -----

3. -----


b. The switch is OFF: 1. -----

2. -----

3. -----

Q4: Decide if the following circuits will work or not:

Understand

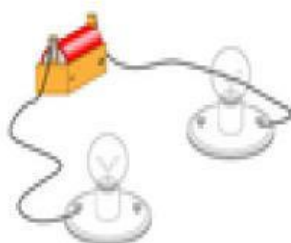

Yes / No



Yes / No



Yes / No

Q5: Write the names of the following components and their function:

Knowledge

Component	Name	Function
		
		
		

Q6: What is the effect of adding:

Analyze

a) More **light bulbs** to the circuit:

b) More **cells** to the circuit:



Scan me!!

The End