

Quantity of Electricity

1. Complete the blanks with the correct answers.

Quantity of Electricity	Unit	Measuring Instrument
Current		
Voltage		

2. Identify the measuring instrument shown below.





3. Based on the diagram shown below, determine how an ammeter and voltmeter is connected in an electric circuit.

