

Name: _____

Class: Year 3 - _____

Day/Date: Monday / 7th September 2026Subject: Science Year 3Topic: **Electrical Circuits****SECTION A**

Read the following sentences. Write "**True**" if the statement is correct and "**False**" if the statement is not correct in the box provided.

NO.	STATEMENT	ANSWER
1.	A complete electrical circuit allows electricity to flow.	
2.	A light bulb can light up when the circuit is incomplete.	
3.	It is safe to touch electrical sockets with wet hands.	
4.	A wires can be used to turn a light bulb on and off.	
5.	We should keep electrical appliances away from water.	

SECTION B

Match the statements in Column A with the correct words in Column C. Write the correct answer in Column B.

COLUMN A	COLUMN B	COLUMN C
1. It provides electrical energy to a circuit	_____	<i>Electricity</i>
2. It is used to turn a circuit on and off.	_____	<i>Dry Cell</i>
3. It produces light when electricity flows through it.	_____	<i>Bulb</i>
4. It is a form of energy that can make electrical appliances work.	_____	<i>Electrical socket</i>
5. We should never put our fingers or objects into this.	_____	<i>Switch</i>

(Total = 10 marks)

Prepared by: Teacher Hazirah