

Name: _____ Class: Year 3 - _____

Day: Monday

Date: 7th September 2026

Science Year 3

Topic: **Electric Circuit**

A. Write down the names of the components below by choosing the correct answers.

Bulb	Switch	Wire	Dry Cell
------	--------	------	----------

1.



2.



3.



4.






Science Year 3

Read the note below carefully:

1. When all the electric components are connected together, the bulb lights up and this is what we call a **Complete Circuit**.
2. Complete circuit makes the bulb light up

B. Choose the correct answer if it is:

Complete Circuit 'OR' Incomplete Circuit

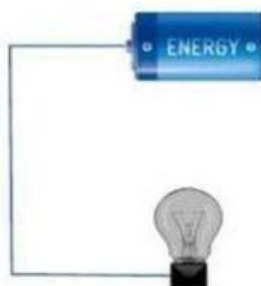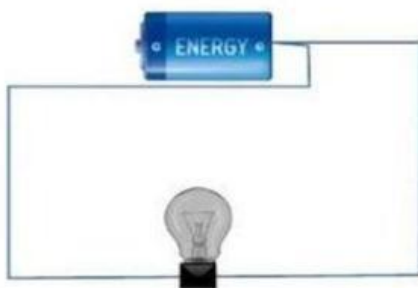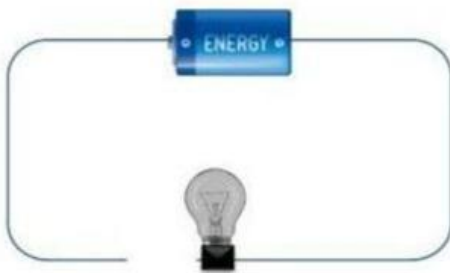

Science Year 3

Look at the circuit below. If you think the bulb will light, write **YES** in the box. If you do not think the bulb will light, write **NO** in the box.

