

Name: _____

Class: _____

Date: _____


Exercise 5.4 Switches

1. Complete the sentences by choosing the correct answer from the choices.

The switch turns the electric _____ on or off. It is the same idea as turning a tap on or off.

_____ a switch completes a circuit and allows electric current to flow.

_____ the switch breaks the circuit.

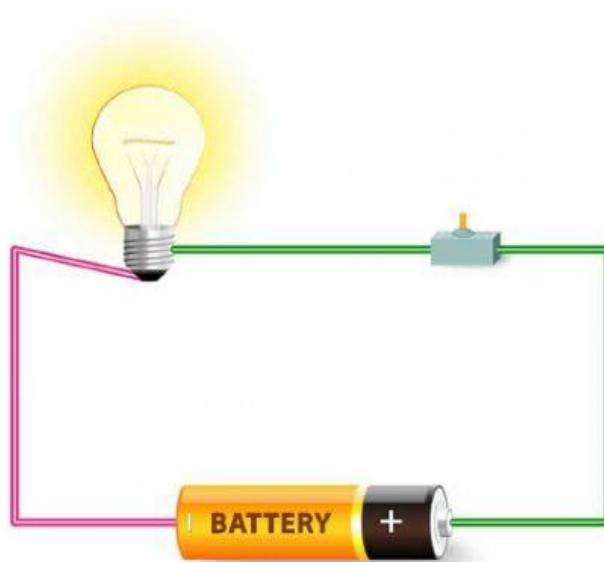

2. Kinds of Switches. Match the picture of the switch to its correct name.

