


Activity 6

Lights Out!


Process skills: Analysing, Inferring

In which circuits will the light bulb light up? Colour the light bulbs that will light up in yellow.


A

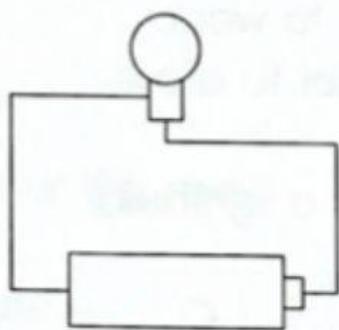


B

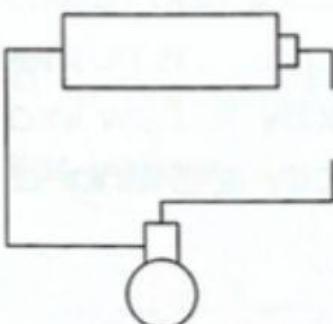


C

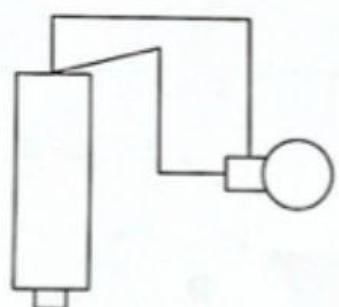

D

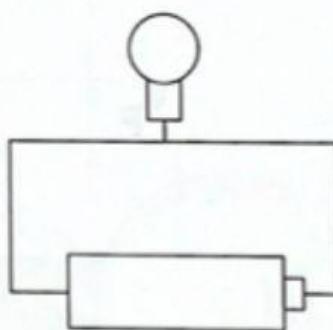

E

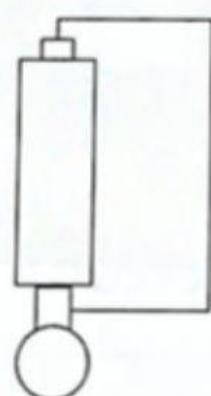

F

