



### SCIENCE EXERCISE 3

Bismillaahirrohmaanirrohiim

Fill in the blanks by using the helping words.

batteries	fires	burns	buzzers	watches
electricity	care	circuit	Shocks	wires
bulbs	mains	kettles	switches	toasters

- Electricity comes from the \_\_\_\_\_ and \_\_\_\_\_ or cells.
- Electricity from the main is used by things such as:
  - Electric \_\_\_\_\_
  - Electric \_\_\_\_\_
- Electricity from battery is used by things such as:
  - Toy cars
  - \_\_\_\_\_
- Electricity flows through a path called a \_\_\_\_\_, which may be made up of:
  - Cells or batteries that push \_\_\_\_\_ around the circuit.
  - \_\_\_\_\_ that close or open the circuit.
  - \_\_\_\_\_ that connect parts of the circuit.
  - \_\_\_\_\_ that use electricity to give off light.
  - \_\_\_\_\_ that use electricity to make sounds.
- Electricity must be use with \_\_\_\_\_ as it can cause:
  - Electric \_\_\_\_\_
  - \_\_\_\_\_
  - \_\_\_\_\_

Alhamdulillahirobbil'alamiin