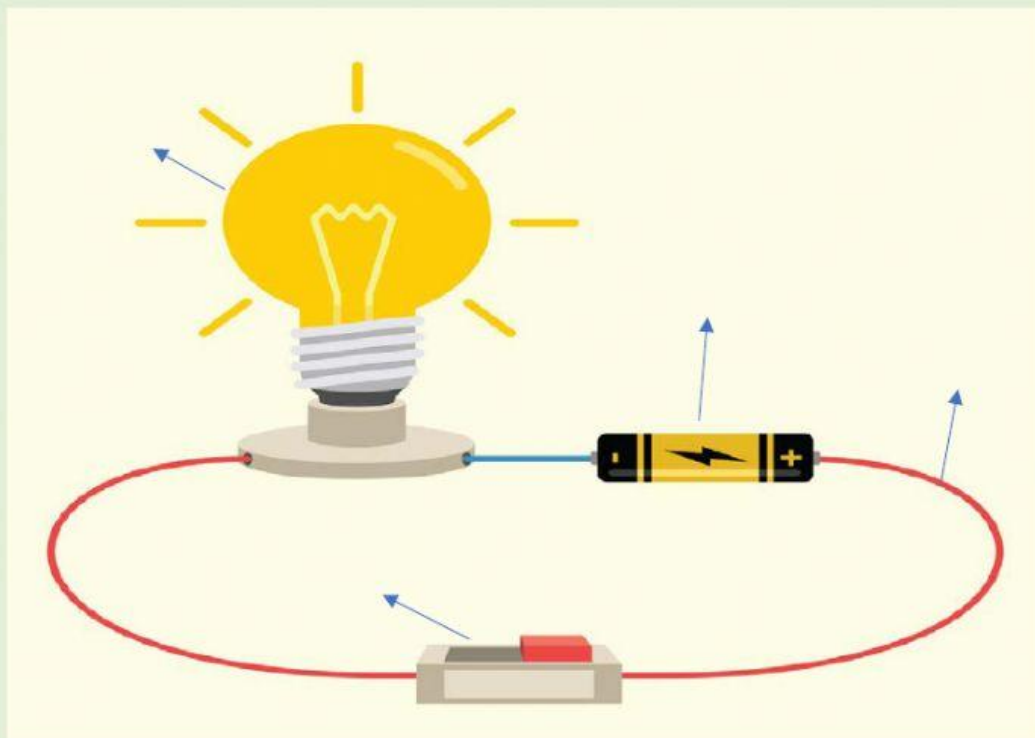


INTRODUCTION TO SIMPLE CIRCUITS

1. After watching the video, label the parts of a simple circuit



2. Complete the statements with the best option:

Wire

Battery

Switch

- _____ provides energy to the circuit
- _____ is the path where the electrons flow through
- _____ opens or closes an electrical circuit

3. Watch the video and complete the statements

- Circuit ____ (**be**) the path through which electricity ____ (**flow**)
- Electricity ____ (**flow**) through the circuit
- Battery ____ (**provide**) the power that causes the electricity to move around the circuit
- Electrons ____ (**flow**) from the negative end to the positive end
- The wires ____ (**provide**) the path that electrons can move through
- The circuit ____ (**work**) when it is closed
- Switches ____ (**be**) components that ____ (**break**) the circuit