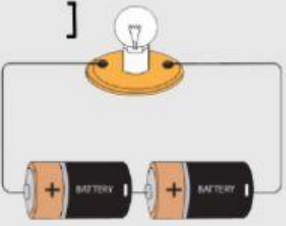
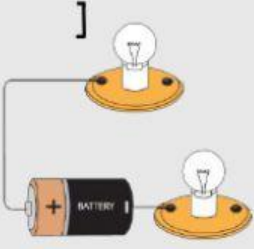
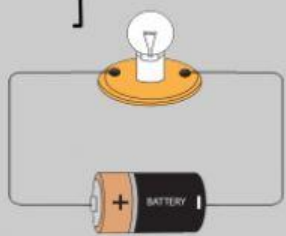
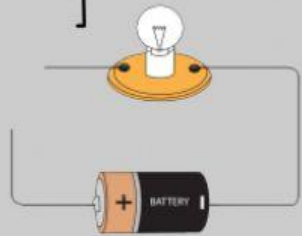
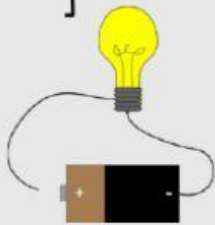
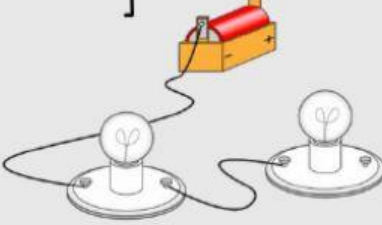
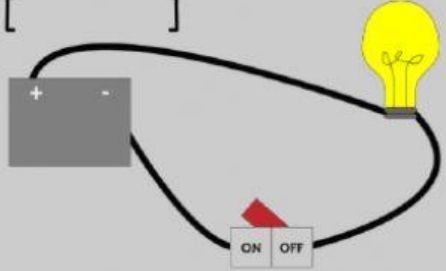
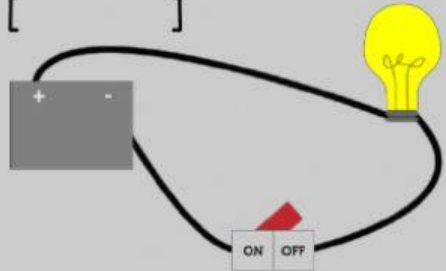
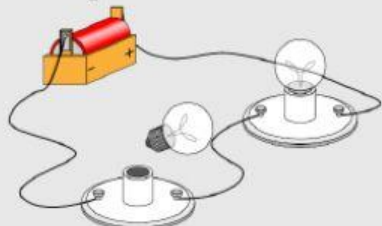


2

SWCS with Micro:bit Lesson 3

DIRECTION: Identify whether a circuit will light up or not?

1. [] 	6. [] 
2. [] 	7. [] 
3. [] 	8. [] 
4. [] 	9. [] 
5. [] 	10. [] 