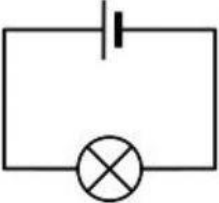
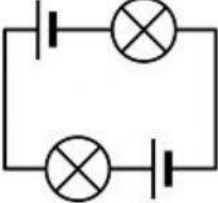
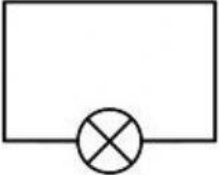
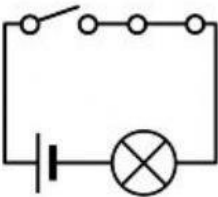
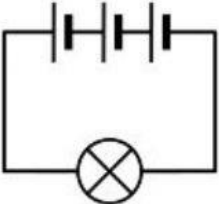
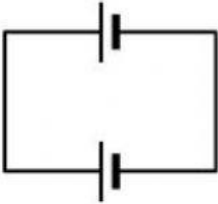
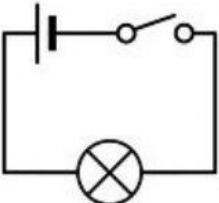
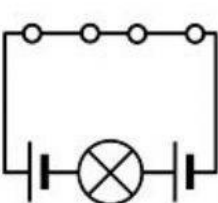
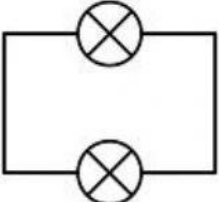
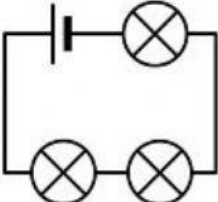
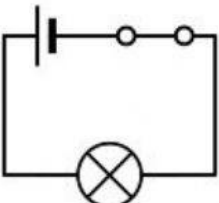
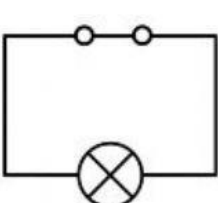


CIRCUIT TESTING

Will the bulbs light in the circuits below?

	☐ Yes ☐ No		☐ Yes ☐ No
	☐ Yes ☐ No		☐ Yes ☐ No
	☐ Yes ☐ No		☐ Yes ☐ No
	☐ Yes ☐ No		☐ Yes ☐ No
	☐ Yes ☐ No		☐ Yes ☐ No
	☐ Yes ☐ No		☐ Yes ☐ No