

Galvanometer Activity

voltmeter

multiplier

shunt

ammeter

very small currents

a galvanometer used to measure?

Connecting a resistance in series with a galvanometer, is the way to convert a galvanometer into _____.

The resistance that is connected in series with a galvanometer is called _____.

The resistance that is connected in parallel with a galvanometer is called _____.

Connecting a resistance in parallel with a galvanometer, is the way to convert a galvanometer into