
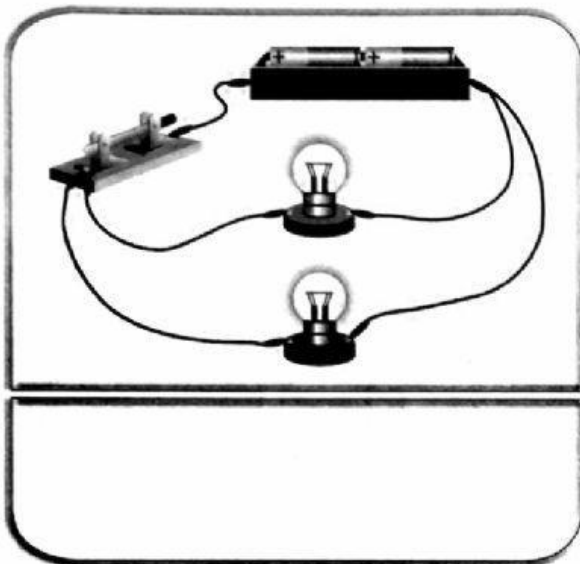


A Write 'Series circuit' or 'Parallel circuit' at the electrical circuits below.


1.

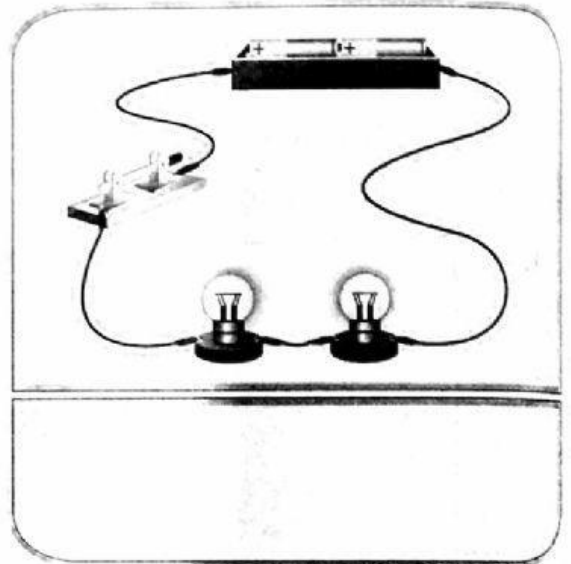


2.




3.

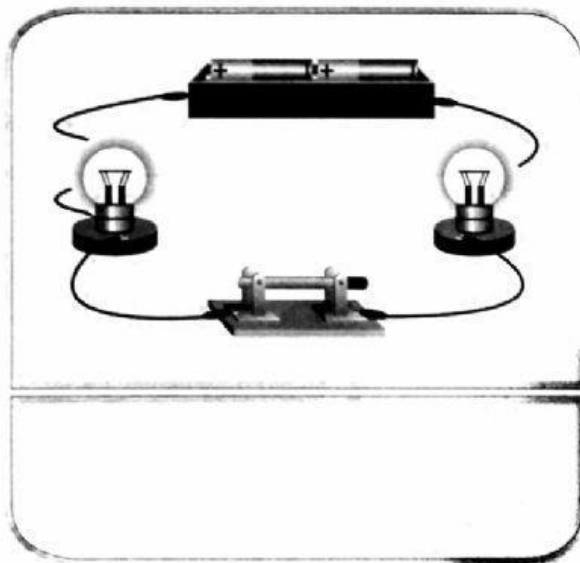

4.

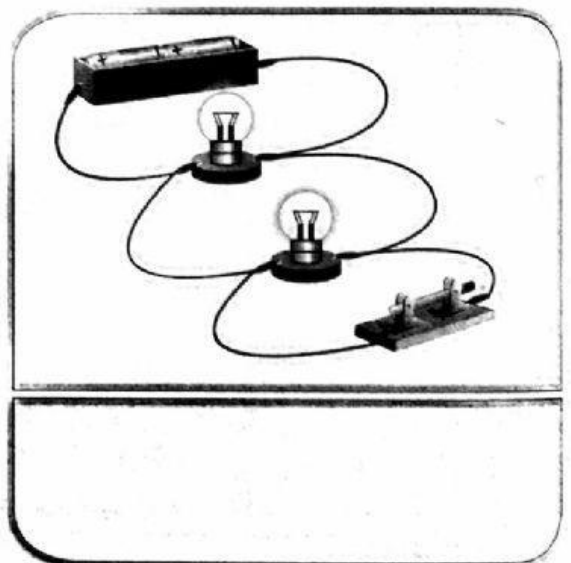

5.

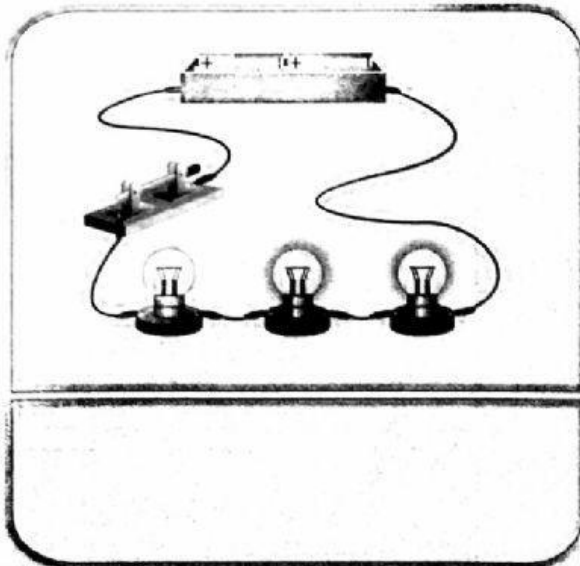

6.

