

UNIT 7 : ELECTRICITY

WORKSHEET 1

Label the components in the electric circuit below.

QPL1

1. <i>_____</i>	Bulb	Connecting wire
2. <i>_____</i>	Switch	Dry cell

