

## 7.1 Electric Circuit

A Name the components found in the electrical circuit below.

SP 7.1.1

Dry cell

Bulb

Switch


Connecting  
wire

1.

2.

3.

4.

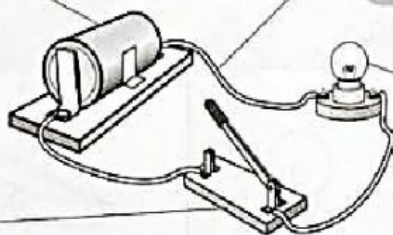

B Match the electrical component to its function.

Complete and break an  
electric circuit.

Supply electrical energy

Produce light

Connect each electrical  
component into a  
complete circuit

