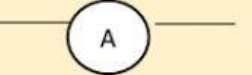
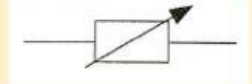
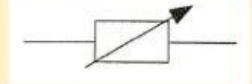


7.2 Pengaliran Arus Elektrik dalam Litar Bersiri dan Litar Selari

1. Padankan komponen elektrik berikut dengan symbol masing-masing

Komponen elektrik		Simbol
a)	Sel Kering	
b)	Ammeter	
c)	Perintang	
d)	Suis	
e)	Voltmeter	
f)	Fius	
g)	Galvanometer	
h)	Perintang boleh ubah	
i)	Mentol	