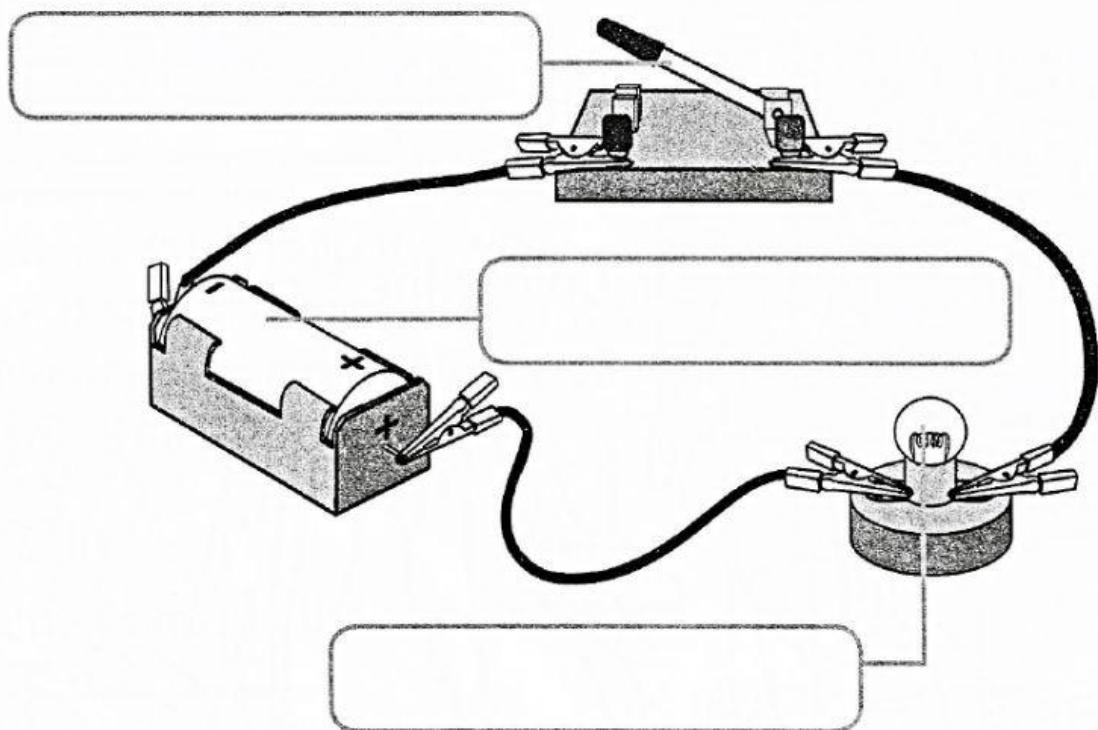


Topic 7.0 Electricity

7.1.1 Identifying Electrical Components

1. Label the electrical components in the circuit below.





2. Tick (✓) the correct answers.


a)





Should be fastened onto

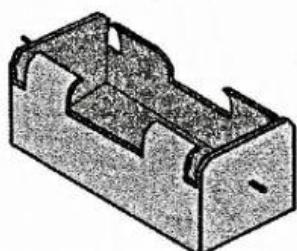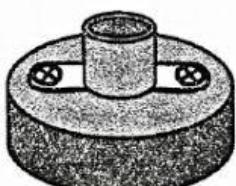

b)

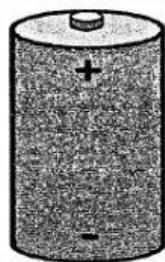


Should be installed in

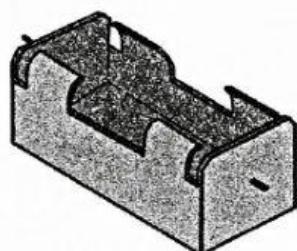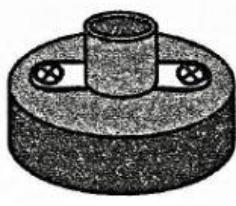


Topic 7.0 Electricity

7.1.2 Functions of the Electrical Components


Match the pictures to their functions.

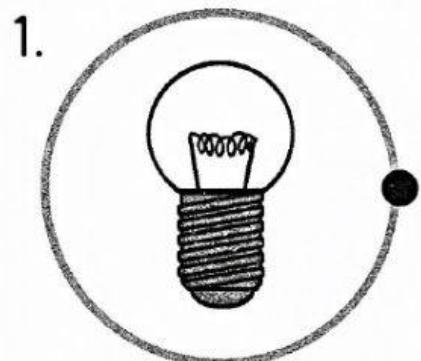


Supply electrical energy

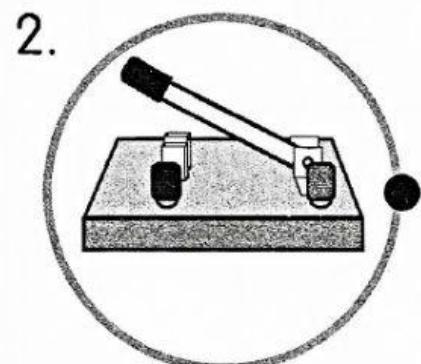

Produce light

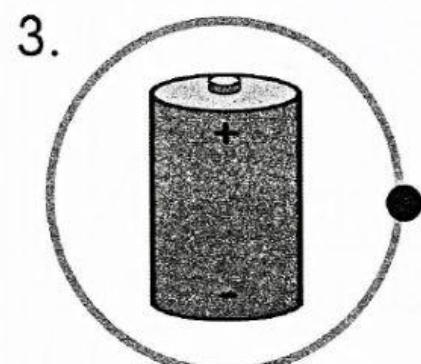

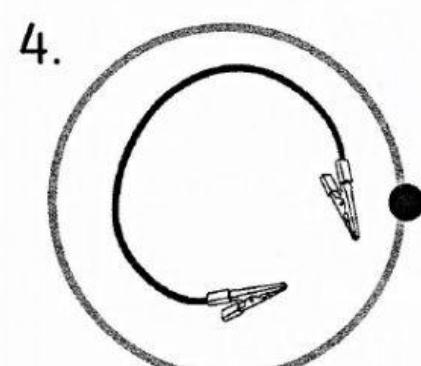Connect components in the electric circuit



Complete and break the electric circuit