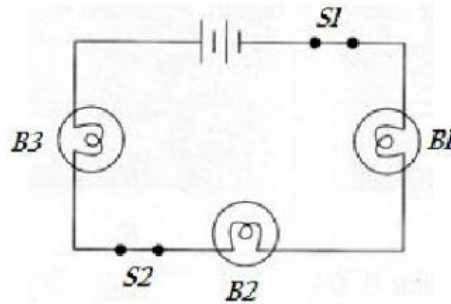


Nama :

Tarikh :

Series circuit



What will happen to the bulbs if :


1. S1 is open and S2 is close -

2. S1 and S2 are close -

3. S1 is close and S2 is open -

Parallel circuit

What will happen to the bulbs if :

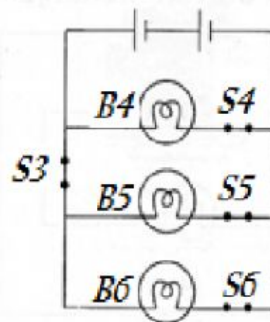

1. S3, S4, S5 and S6 are close -

2. S3 is open. S4, S5 and S6 are close -

3. S5 is open. S3, S4 and S6 are close -

4. S6 is open. S3, S4, S5 are close -

5. S4 and S5 are open. S3 and S6 are close -