
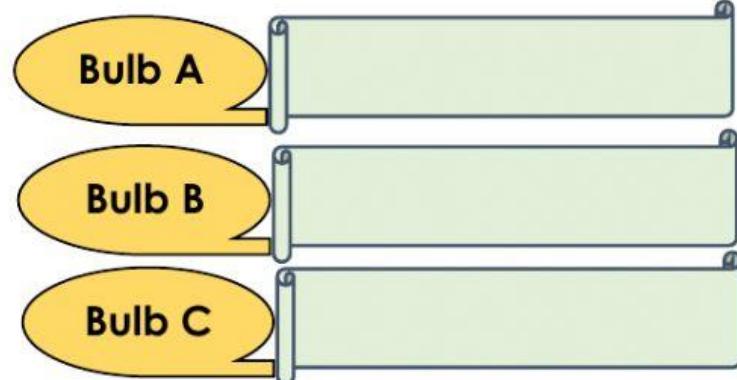


Conclude the factors that affect the bulbs in series and parallel circuits based on the opened switch or closed switch



TP 5

1. Observe and study the condition of switches based on the diagrams given below. State the conditions of the bulbs. Write lights up or does not light up

Circuit 1

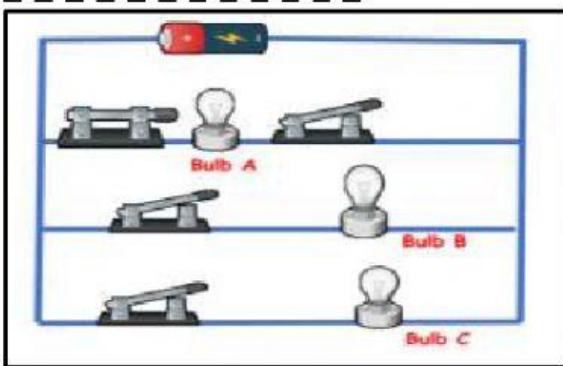

Circuit 2

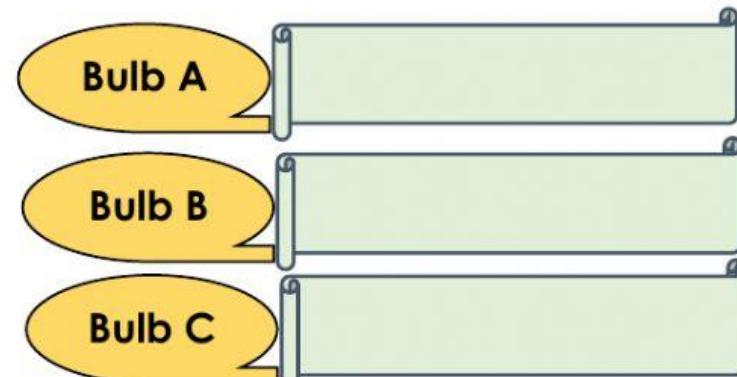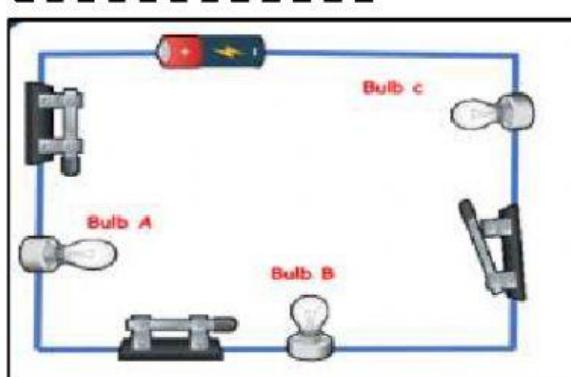

Circuit 3

