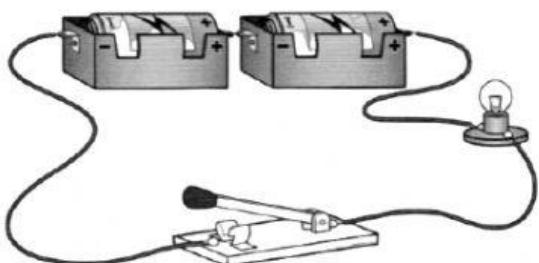



Find out why the bulbs in the pictures below do not light up,  
and match to the correct reason.

请找出以下图片中灯泡没有亮起的原因，并配对正确的答案。




The dry cell is out of energy

干电池的电量耗尽

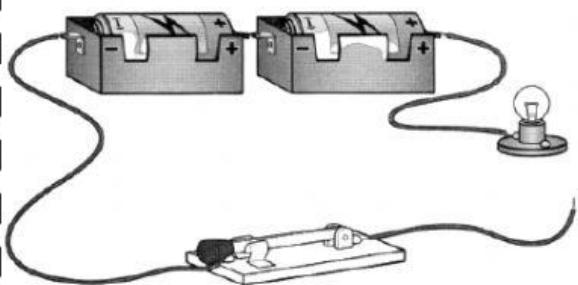

The wire is not connected to the components

电线没有连接到元件

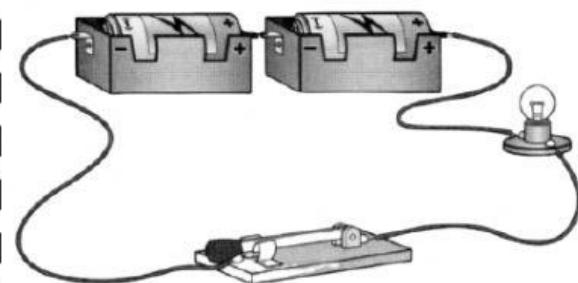

The bulb is not fastened properly into the holder

灯泡没有被正确旋入灯泡座

The switch is opened

开关被拉上了