

Thursday




5 August 2021

Electricity

Building An Electric Circuit

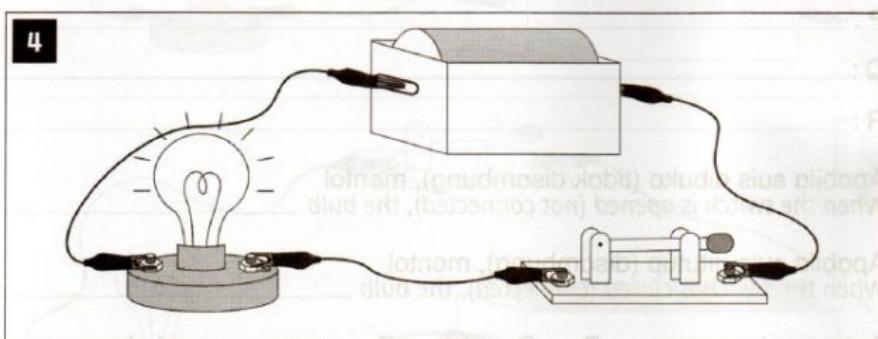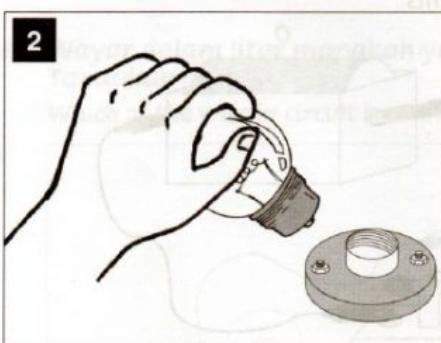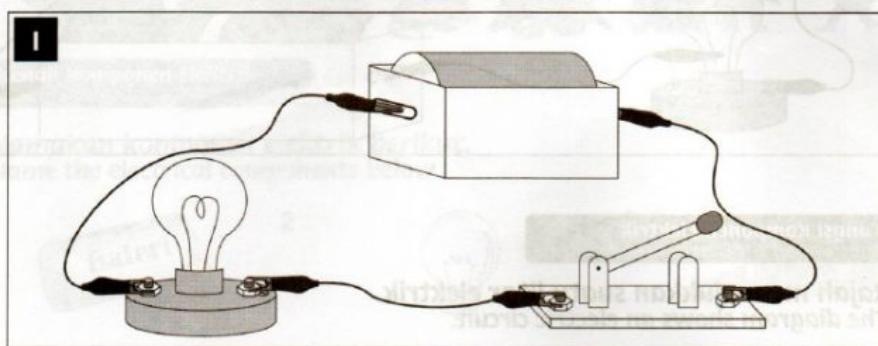1. The following is the steps to build an electric circuit. Arrange according to the correct sequence. Label 1,2,3 and 4 in the blanks.







Berikut ialah langkah-langkah membina litar elektrik. Susun mengikut urutan yang betul. Labelkan 1,2,3 dan 4 di ruang kosong.



2	→	3	→	1	→	4
---	---	---	---	---	---	---

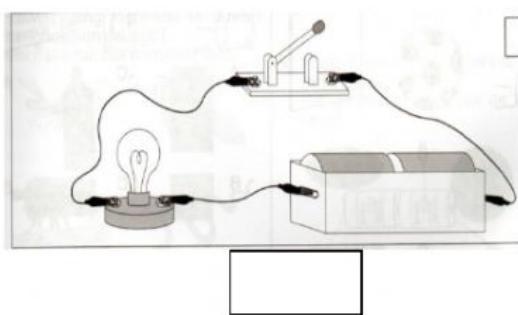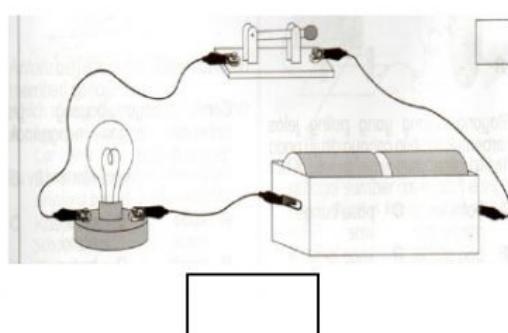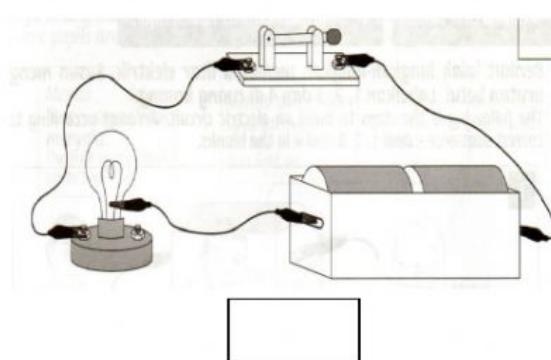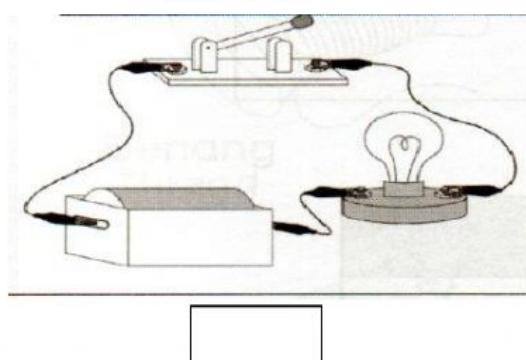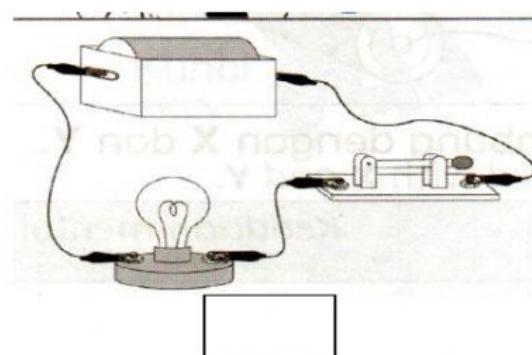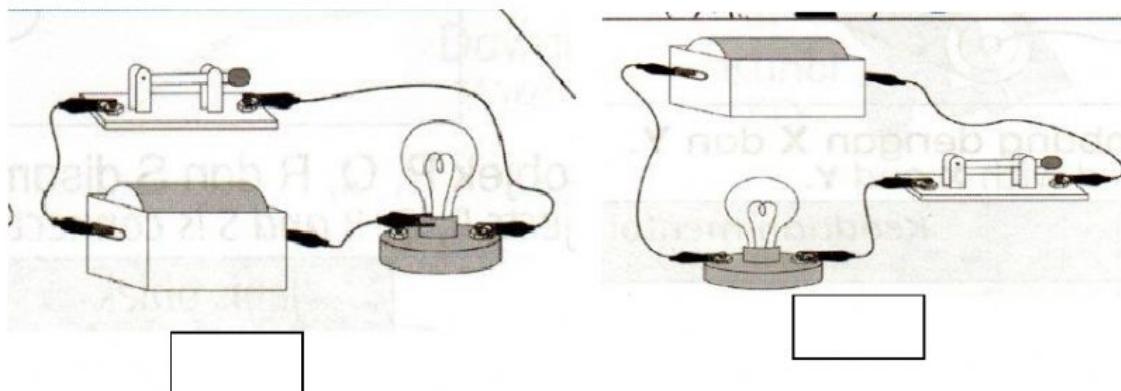2. Which of the wire in circuit is connected correctly? Tick / for the bulb light up and X for not light up.

Wayar dalam litar manakah yang dipasang betul? Tandakan / mentol yang beryala dan X tidak beryala.



3. i. When the switch is opened (not connected), the bulb _____
Apabila suis dibuka (tidak bersambung), mentol _____

ii. When the switch is closed (connected), the bulb _____
Apabila suis ditutup (bersambung), mentol _____