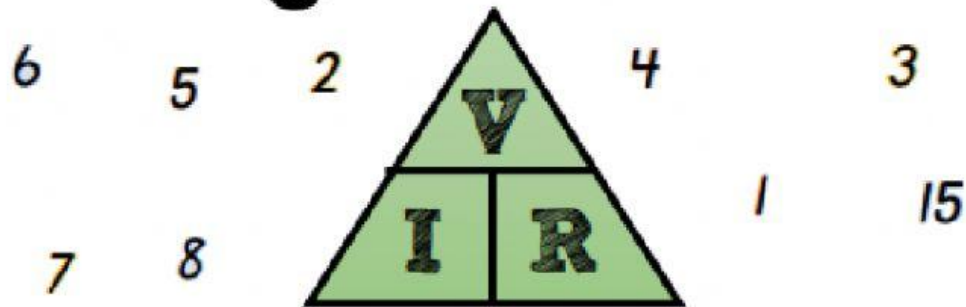


Pengiraan Ohm



Volta (V)	Arus (I)	Rintangan (Ω)
	2	3
4	2	
12		12
	4	2
15	5	
20		5
	3	5
28	4	
10		2