

Date :(Thursday)





Name :

Science Year 2

Class :

ELECTRICITY : BUILDING AN ELECTRIC CIRCUIT

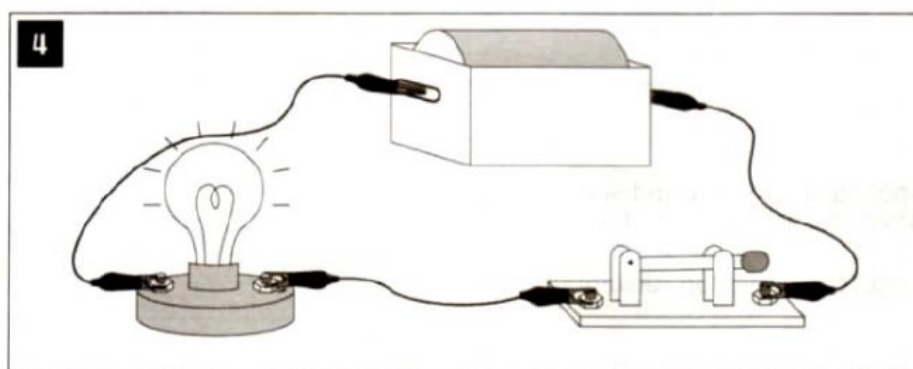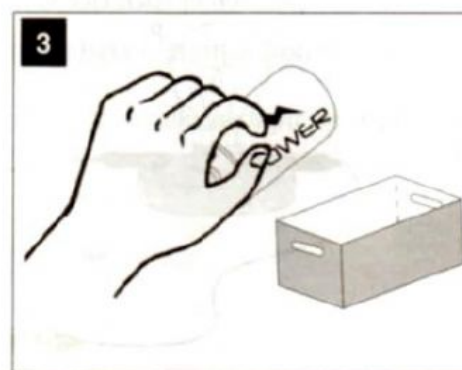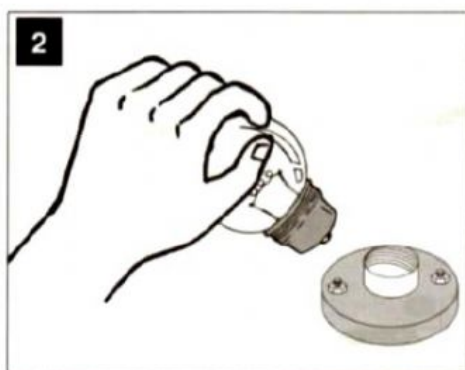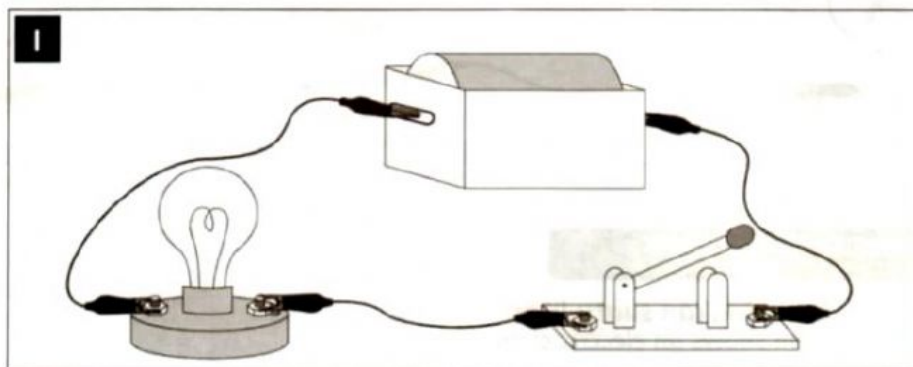1. The following is the steps to build an electric circuit. Arrange according to the correct sequence. Label 1,2,3 and 4 in the blanks.



<input type="text"/>	→	<input type="text"/>	→	<input type="text"/>	→	<input type="text"/>
----------------------	---	----------------------	---	----------------------	---	----------------------


Date :(Thursday)

Name :

Science Year 2

Class :

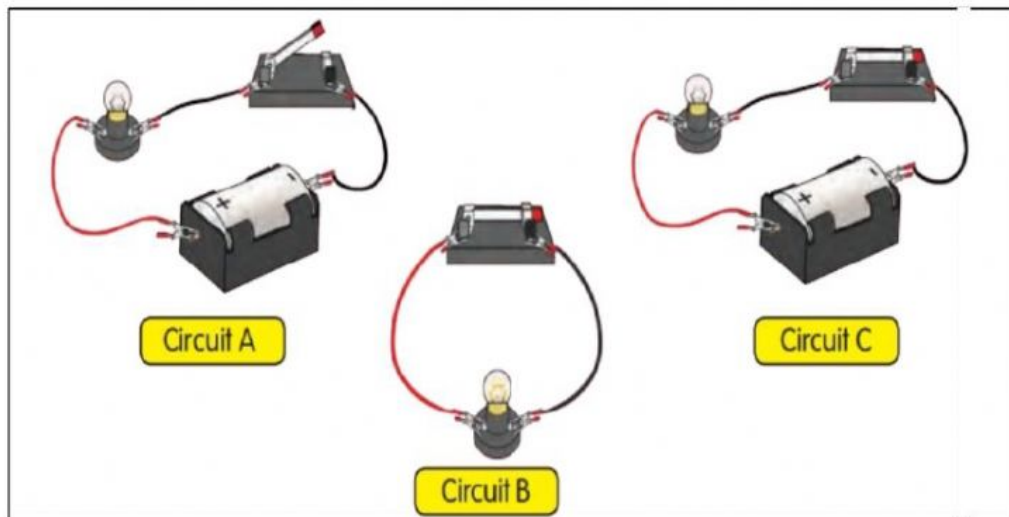2. Observe the circuit. Answer question 2a to 2d is based on the diagram below.



- a. Which bulb will light up?

- b. Why does the bulb in that circuit light up?

The bulb light up because the circuit is _____.

- c. Which bulb will not light up?

- d. Why does the bulb in that circuit light up?

The bulb not light up because the circuit is

_____.