
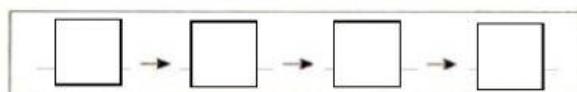
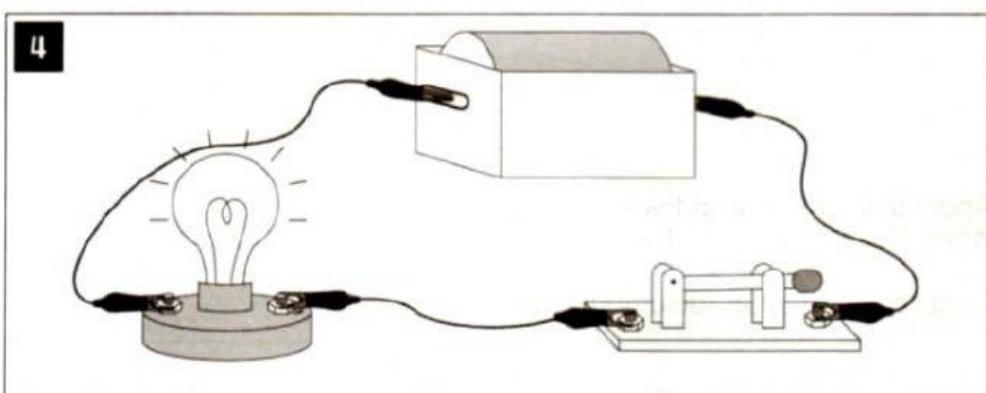
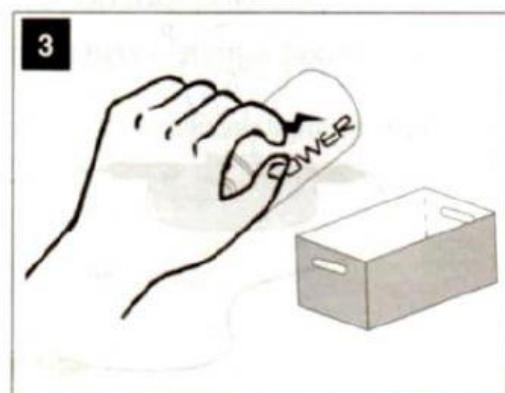
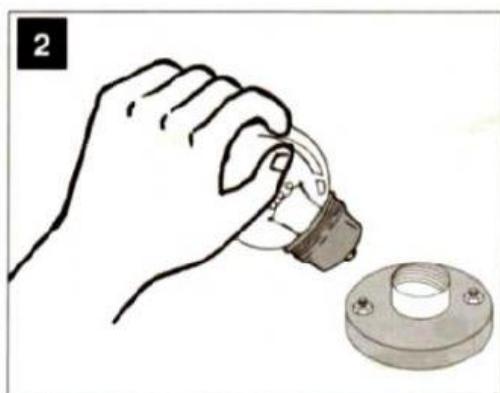


Date :(Thursday)


Name : Science Year 2 Class :

ELECTRICITY : BUILDING AN ELECTRIC CIRCUIT

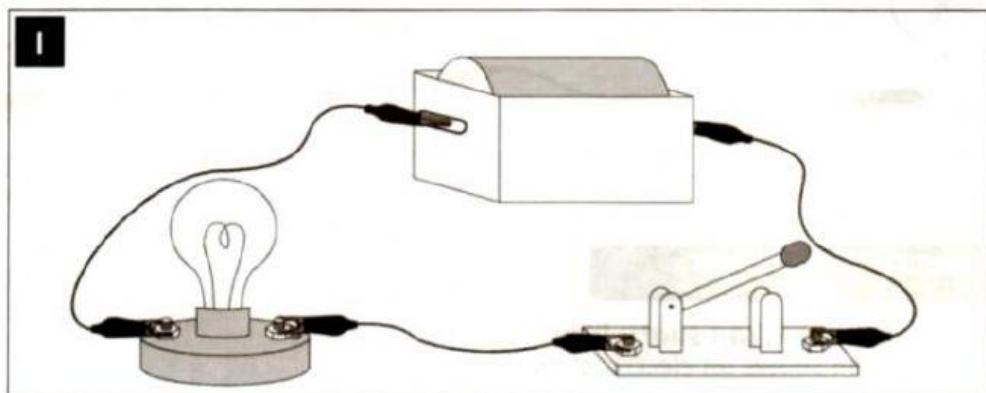1. The following is the steps to build an electric circuit. Arrange according to the correct sequence. Label 1,2,3 and 4 in the blanks.



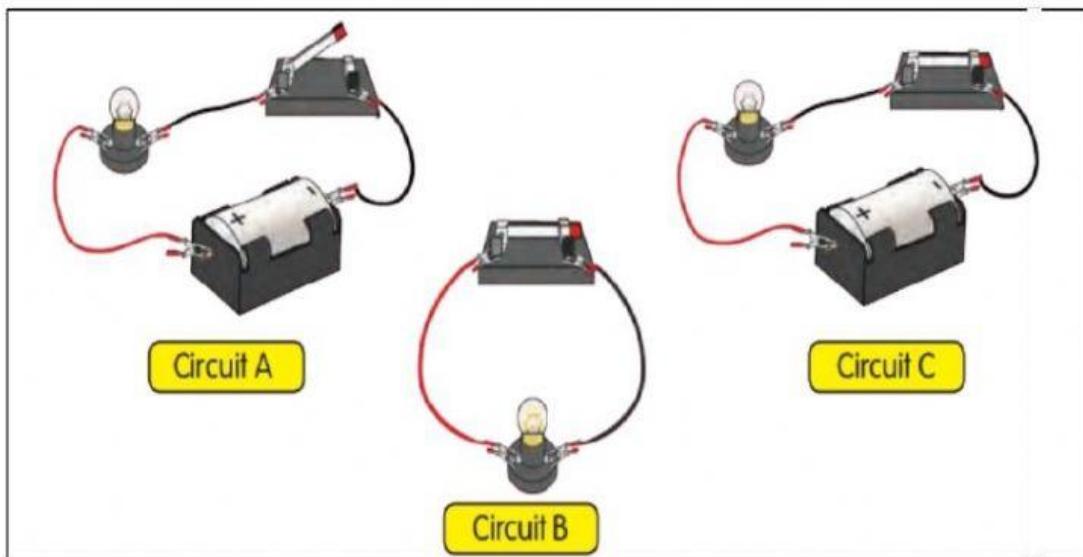2. Observe the circuit. Answer question 2a to 2d is based on the diagram below.



a. Which bulb will light up?

b. Why does the bulb in that circuit light up?

The bulb light up because the circuit is _____.

c. Which bulb will not light up?

d. Why does the bulb in that circuit light up?

The bulb not light up because the circuit is
