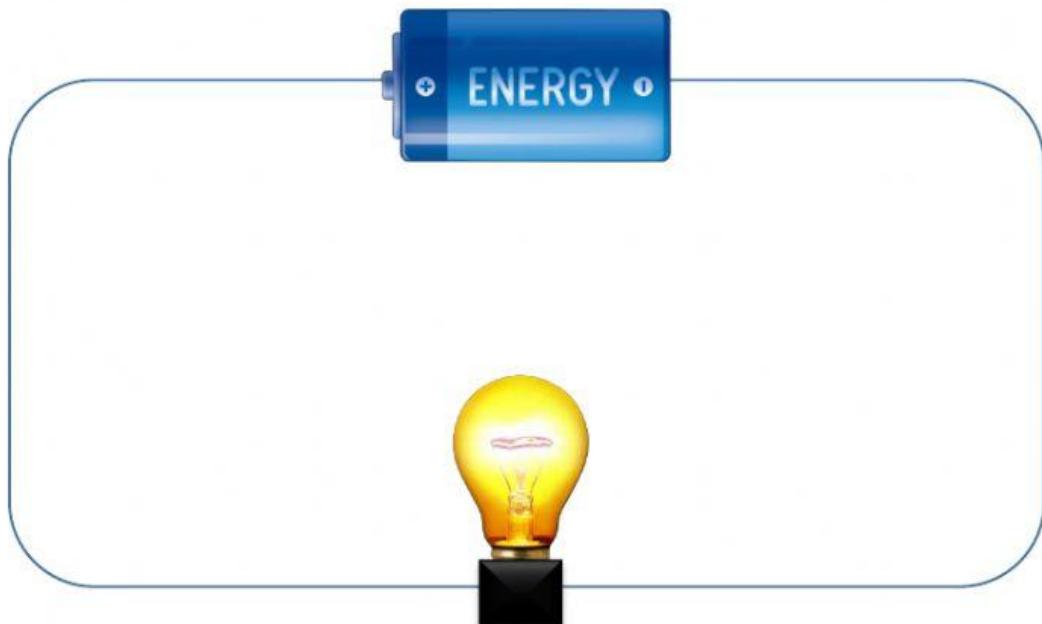


Science Year 3

Complete Circuit and Incomplete Circuit.

Read the note below carefully.




Look, at the picture carefully.

1. Do the bulb light up?

2. When all the electric component are connected together

the bulb light up and this is what we call **Complete Circuit**.

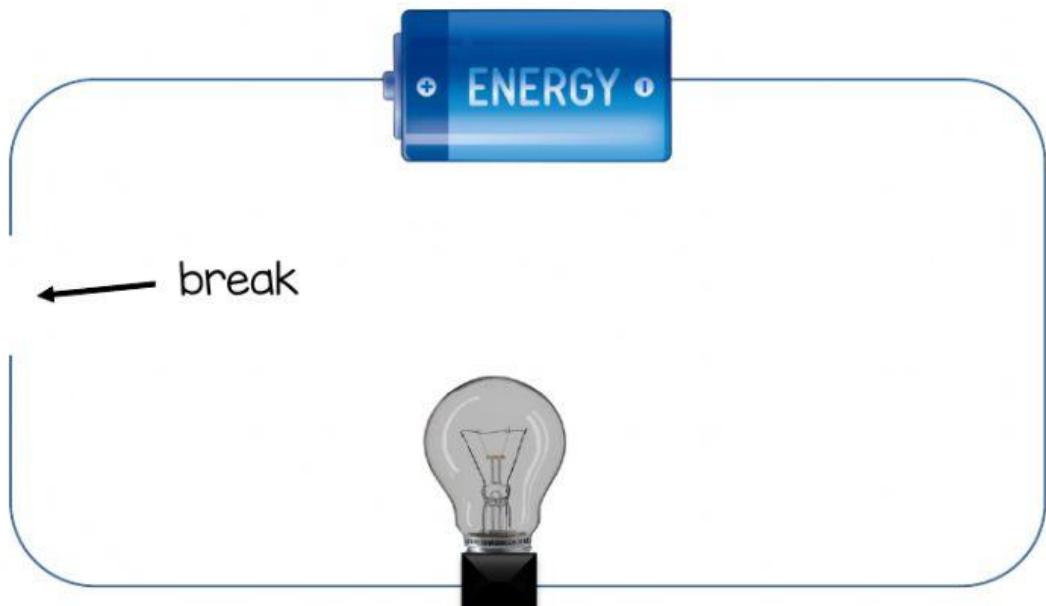3. **Complete circuit** make the bulb lights up.



Look, at the picture carefully.

1. Do the bulb light up?

2. When there is a **break**, the wire are not connected. The bulb do not light up and this is what we called **Incomplete Circuit**.

3. **Incomplete circuit** do not make the bulb lights up.

Science Year 3

Choose the correct answer if it is **Complete Circuit** or **Incomplete Circuit**

