
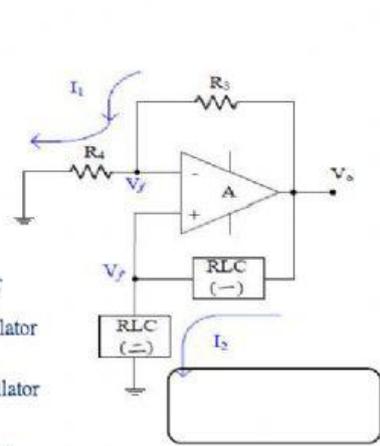



What converts a DC signal into and AC signal at a predetermined frequency?

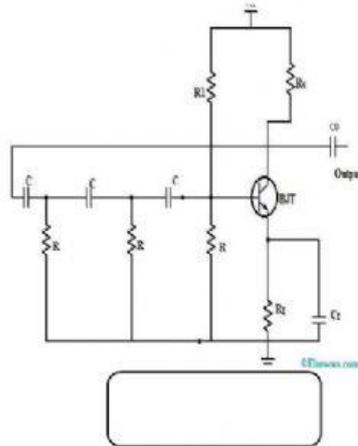1. Transistor
2. Zener Diode
3. Oscillator
4. Thyristor

Multivibrator
 phase-shifted oscillator
 Wien-bridge oscillator





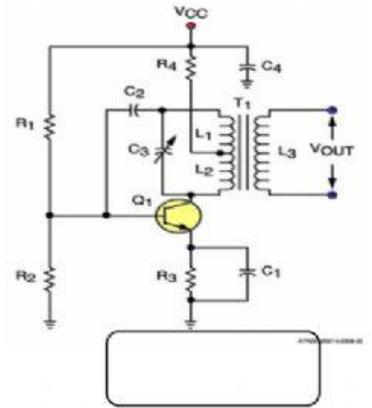

Hartley oscillator
 Colpitts oscillator
 Pierce oscillator

Name

No.

