







Name \_\_\_\_\_ Date \_\_\_\_\_

LO – To be able to work with electrical circuits


AC 1.2 Identify simple circuits in which electricity can flow  
AC 3.1 – To build simple working circuits

Instructions:

1. Make a prediction on whether the circuit will work
2. Build the circuit and check your prediction

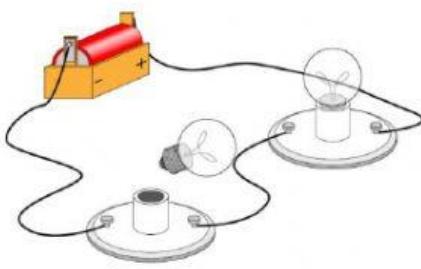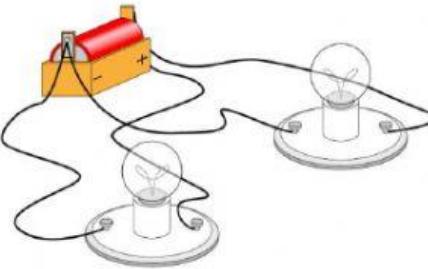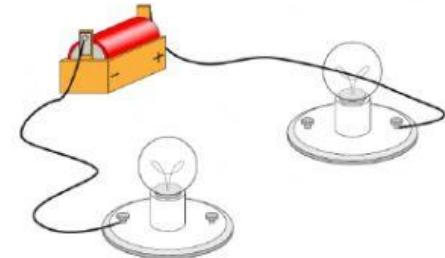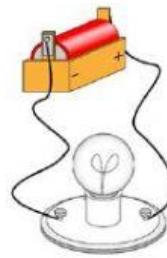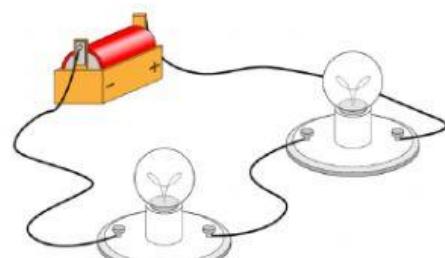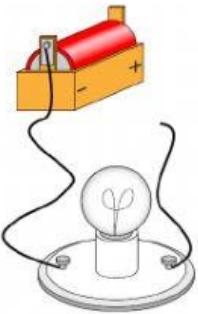
<p>1. Will it work? <b>YES</b> <b>NO</b></p>  <p>Did it work? <b>YES</b> <b>NO</b></p>	<p>2. Will it work? <b>YES</b> <b>NO</b></p>  <p>Did it work? <b>YES</b> <b>NO</b></p>
<p>3. Will it work? <b>YES</b> <b>NO</b></p>  <p>Did it work? <b>YES</b> <b>NO</b></p>	<p>4. Will it work? <b>YES</b> <b>NO</b></p>  <p>Did it work? <b>YES</b> <b>NO</b></p>
<p>5. Will it work? <b>YES</b> <b>NO</b></p>  <p>Did it work? <b>YES</b> <b>NO</b></p>	<p>6. Will it work? <b>YES</b> <b>NO</b></p>  <p>Did it work? <b>YES</b> <b>NO</b></p>

7. Will it work? **YES** **NO**

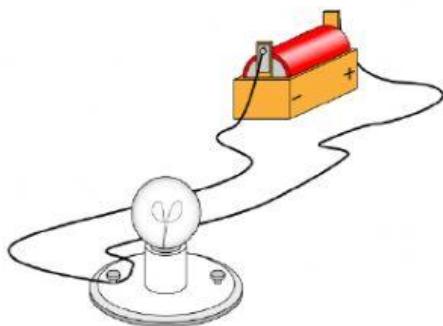

Did it work? **YES** **NO**

8. Will it work? **YES** **NO**

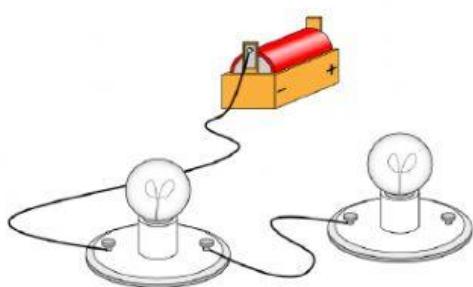

Did it work? **YES** **NO**

Green/Yellow/Red

I/S/L