




Nusa Jaya School 2021

Year 3A

Date:

TOPIC: Using a switch

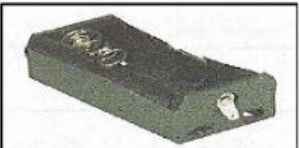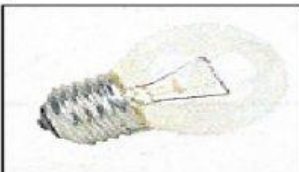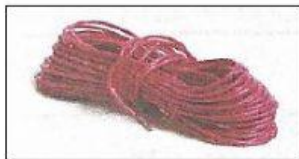(1) Match part of the electric circuits below with their correct names.



light bulb holder

dry cell holder

light bulb

wires

dry cell

(2) What happened when you turned the switch to the 'on' position? Why did this happen?

(3) What happened when you turned the switch to the 'off' position? Why did this happen?

(4) What is a switch used for?