


School name.....

Student Name.....Student No.....Class

REF02002

Installing domestic refrigeration systems compression systems

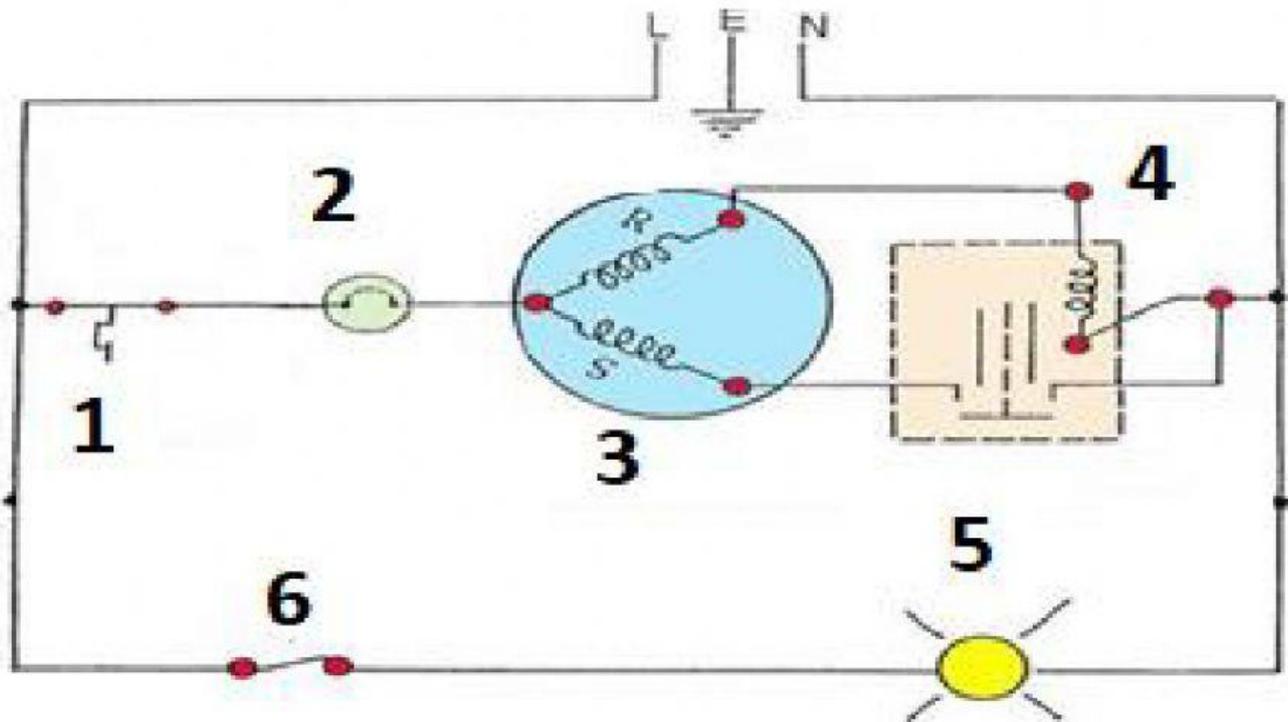Complete the table below after study the figure shown



Wiring diagram of single door fresh food refrigerator

No	Name	No	Name
1		4	
2		5	
3		6	

compressor motor

Thermostat

Overload

Lamp

Lamp switch

Current coil relay