

Name : _____

Switch


Label the picture below using the given words

Dry cell

switch

wire

light bulb

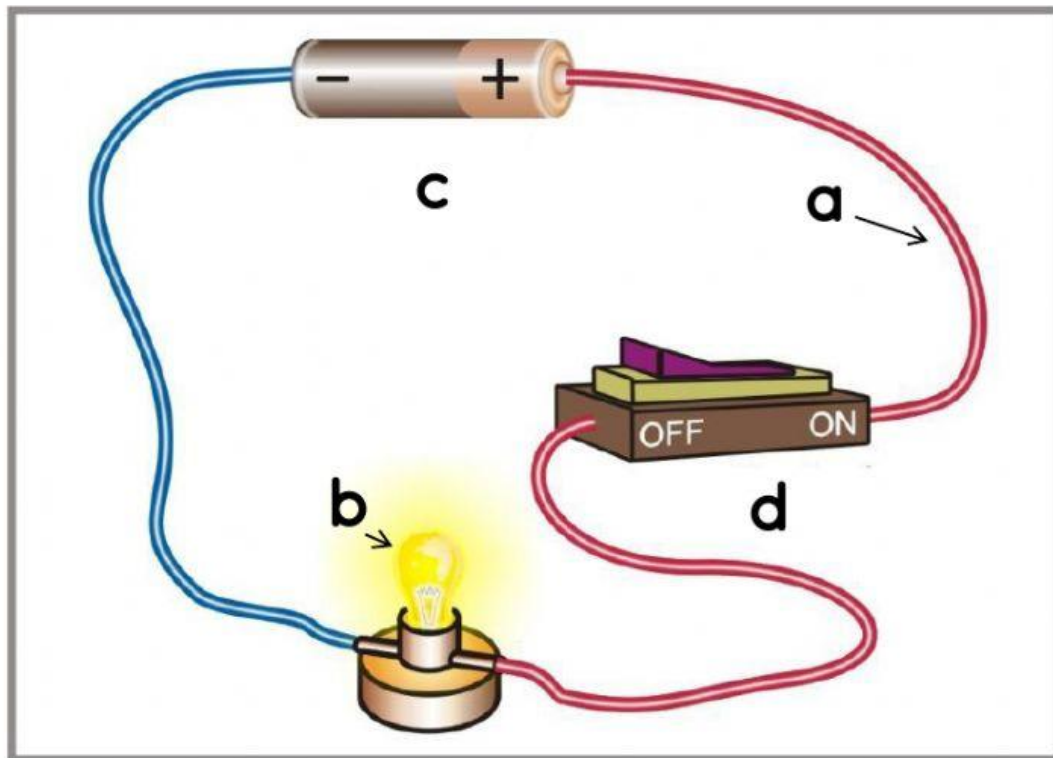

(a) _____

(b) _____

(c) _____

(d) _____

Match you answer.




dry cell



wires




light bulb

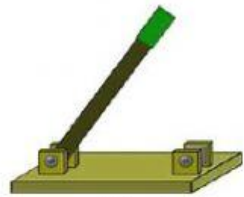


switch

	can make or break the circuit
	provide light
	Supply electrical energy
	Carries current to the other parts of the component

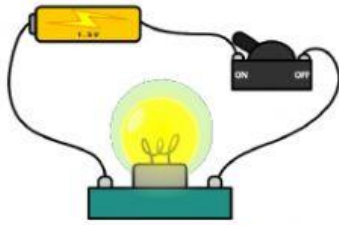Which bulb will light up? Choose Yes or No




1.

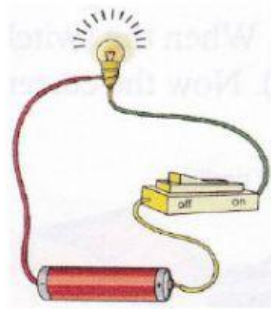☐


2.

☐

3.

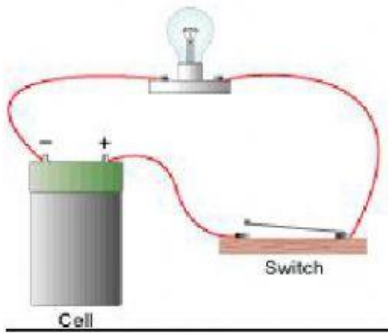☐

4.

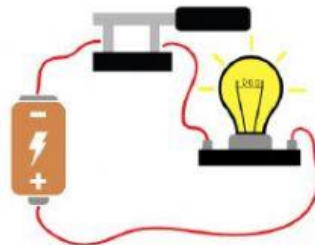☐


5.

☐

6.

☐

7.

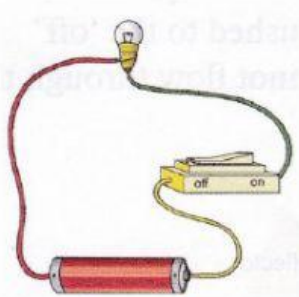☐

8.

☐