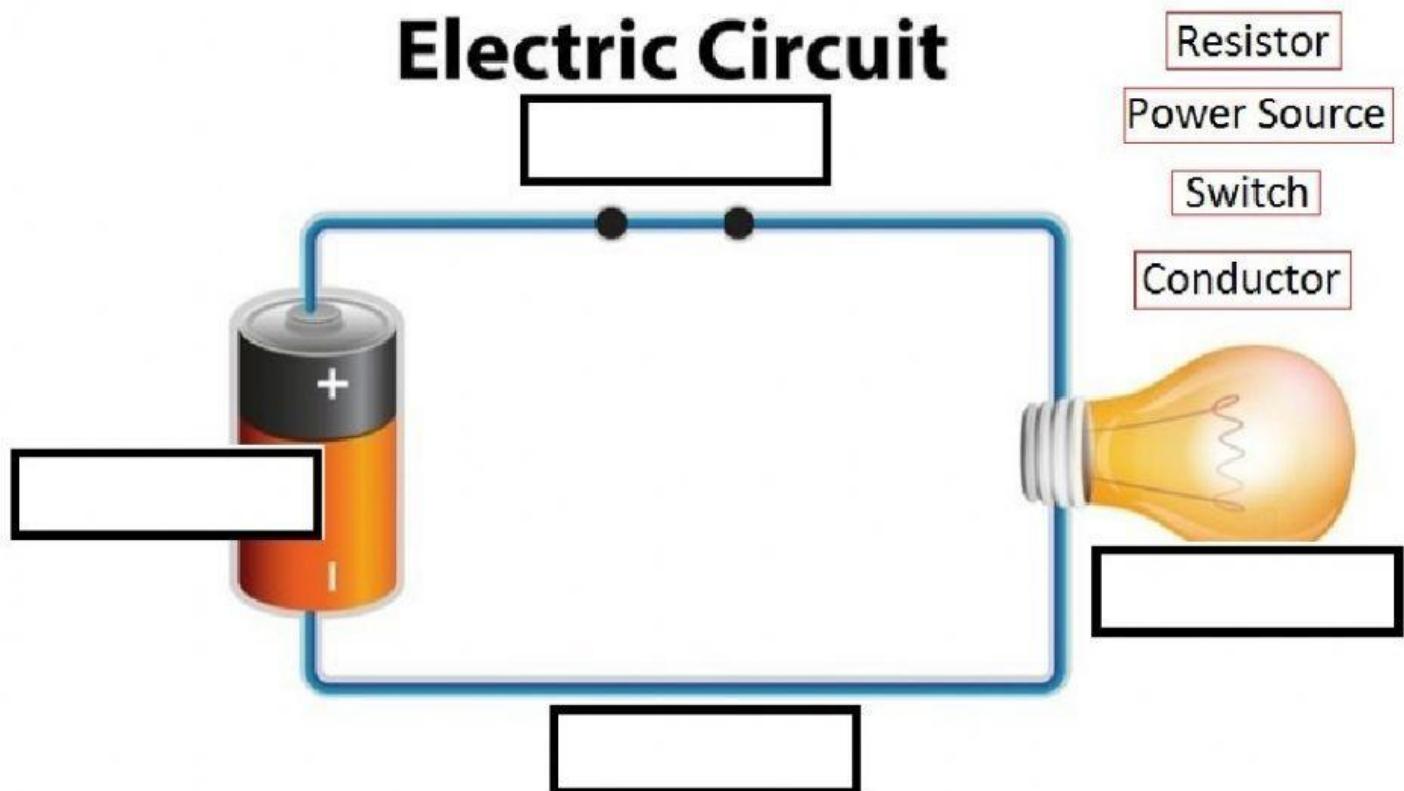


# ELECTRICAL CIRCUIT

A) Drag and label the elements of the electrical circuit.



B) Match the elements to the definitions.

RESISTOR	• It generates the energy.
CONDUCTOR	• It opens or closes the circuit.
POWER SOURCE	• It converts electricity in another type of energy.
SWITCH	• Electricity flows through this element.