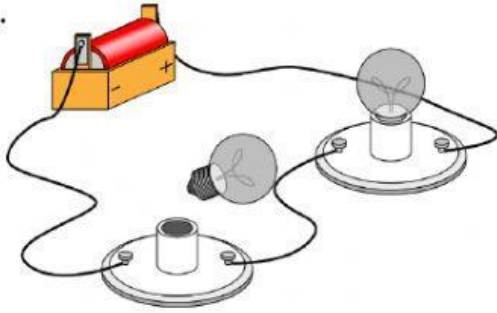


Name: _____


Electrical Circuits

Tell whether the light bulb or bulbs will light or will not light based on the circuit.


1.




2.

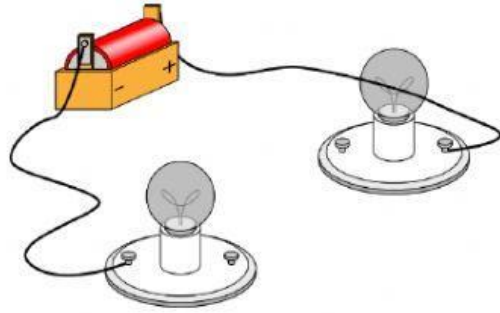


3.

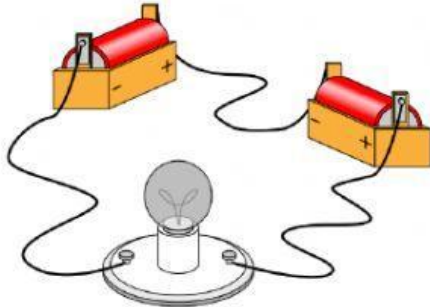

4.

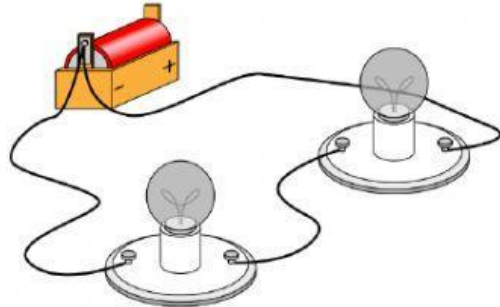

5.

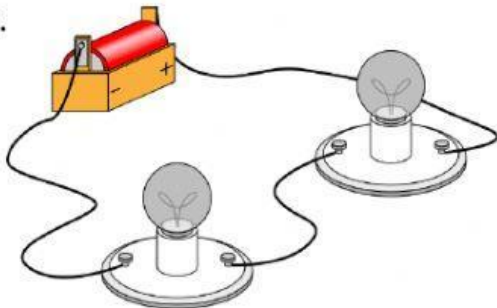

6.

