

Applied English

Unit 4 – Cause and Effect

Review of Week 2 Term 2

Switches and Relays

1. Drag and drop the electronic symbol words under the correct images below.

conductor

lamp

buzzer

bell






battery

terminal

earth

switch

fuse

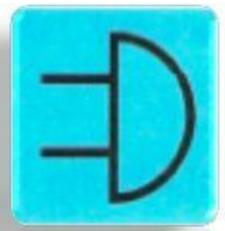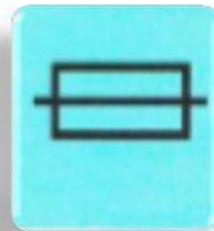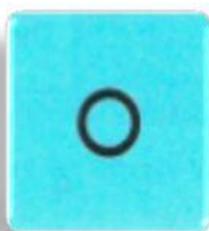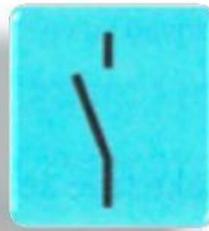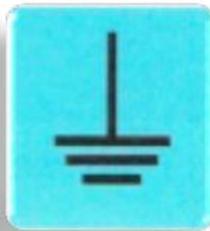

2. Label the two diagrams below with the correct words from the box.

battery



buzzer

spring

switch

terminal

wire

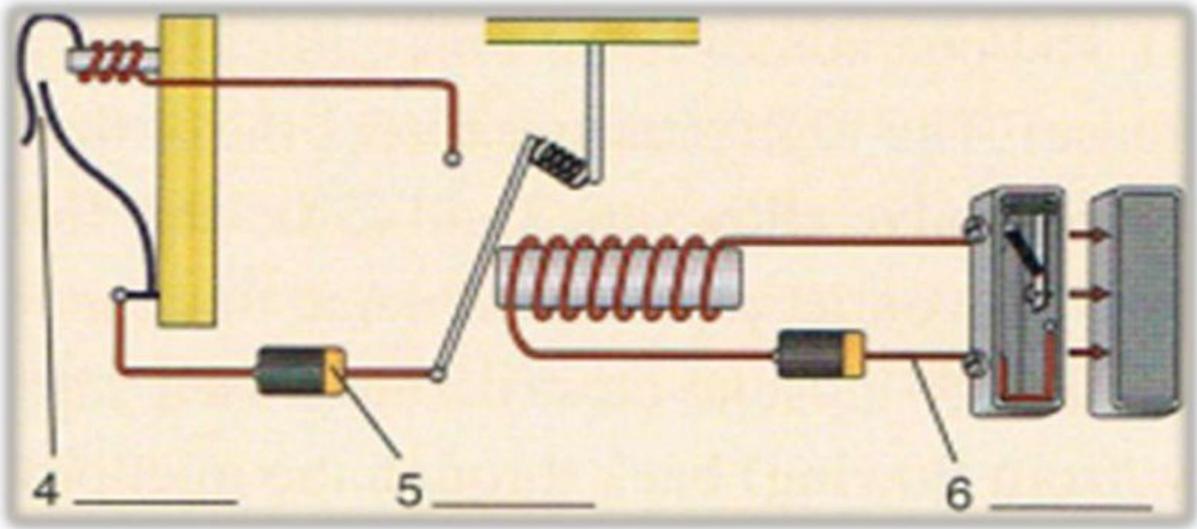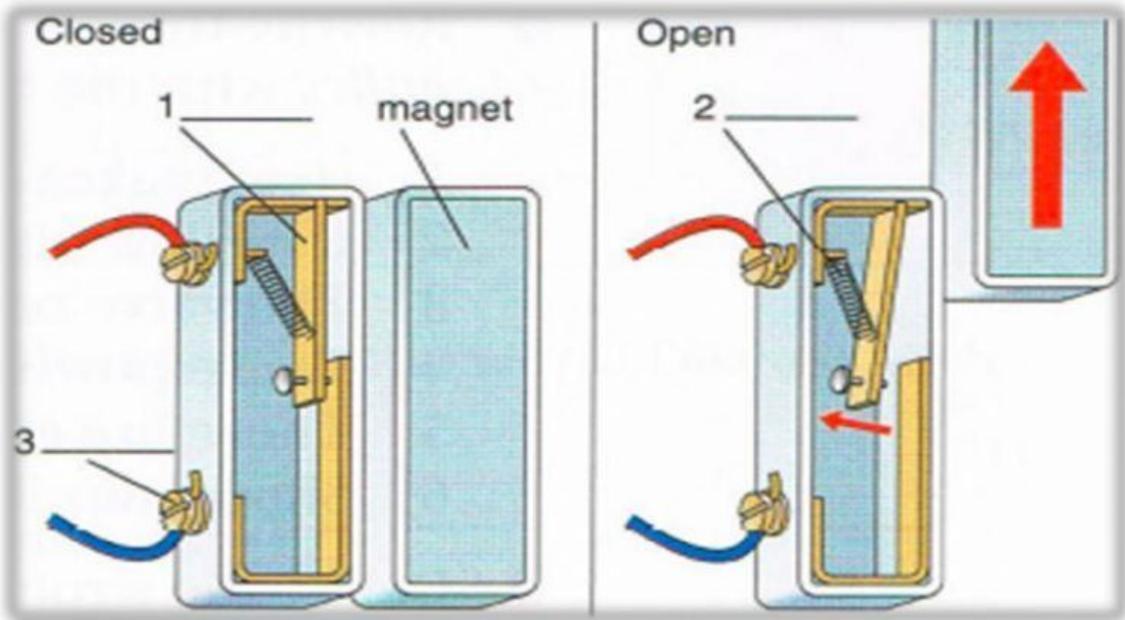

3. Label the parts of a circuit breaker with the correct words from the box.

terminal

fixed
contact

switch

moving
contact

electro-
magnet

terminal

catch

