

LET'S ANSWER - ELECTRICAL CIRCUIT

1:00




W 1- U- What is electricity






Activity 1.1.4



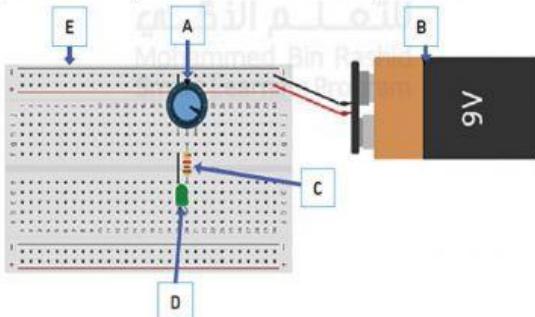Study the electric circuit given below and then answer the questions below.



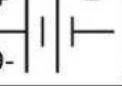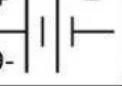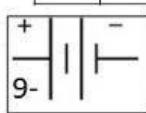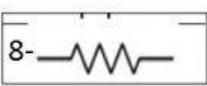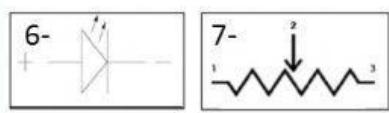1- Battery 2- Breadboard 3- Potentiometer 4- Resistor 5- LED



Name:

Class:



LIVE WORKSHEET

Share your answer in the chat box

Label	Component name	Schematic symbol
A		
B		
C		
D		
e		