

Worksheet 5.3c

Make a bulb light up

Name: _____ Date: _____

Make circuits you have used. Cut and stick the bulbs and cells. Then draw the wires.

() _____	() _____
() _____	() _____

This circuit	did	did not	work.
The bulb	lit up.	did not	light up.

