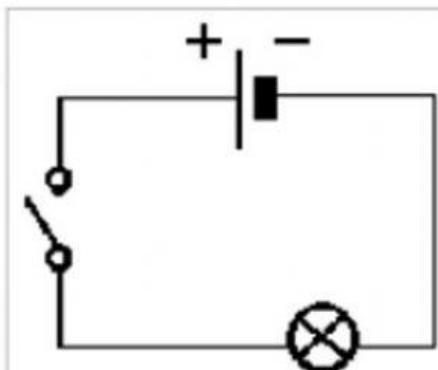




## Activity 9




Look at these circuit diagrams. Which will work? Which need repairs?




Bulb On

Bulb Off

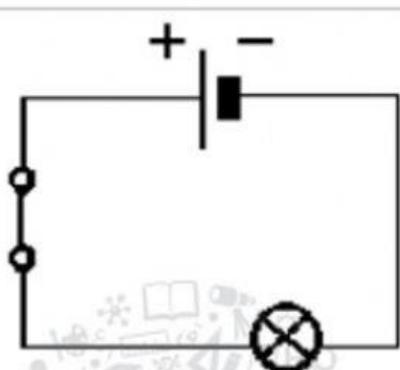


Bulb On

Bulb Off

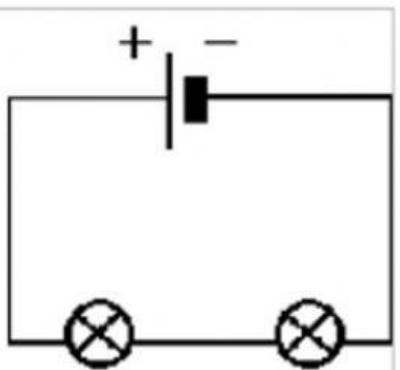


Bulb On

Bulb Off

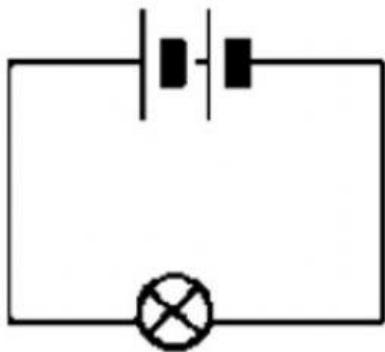


Bulb On

Bulb Off

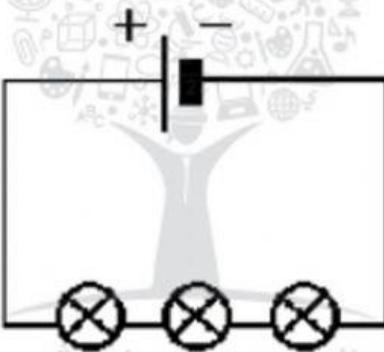


Bulb On

Bulb Off

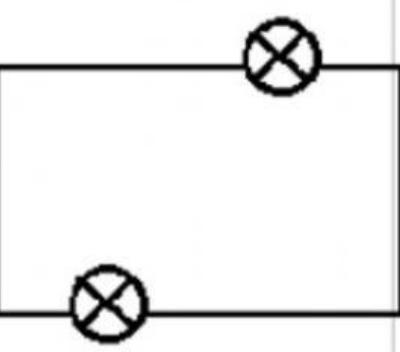


Bulb On

Bulb Off

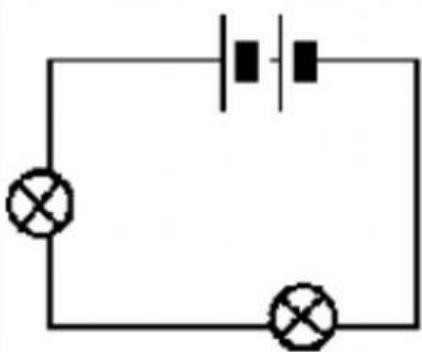


Bulb On

Bulb Off

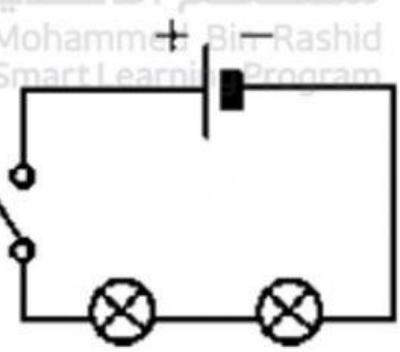

Bulb On

Bulb Off

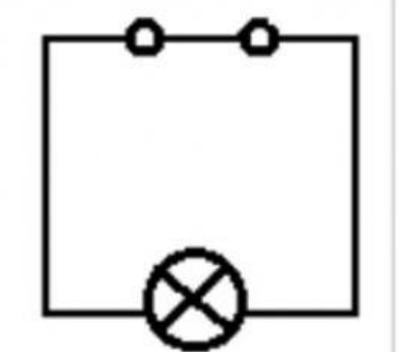

Bulb On

Bulb Off

