

Name : _____ Grade: _____

Activity 9 : Look at the circuit carefully and answer whether the light bulb will be On or Off

