
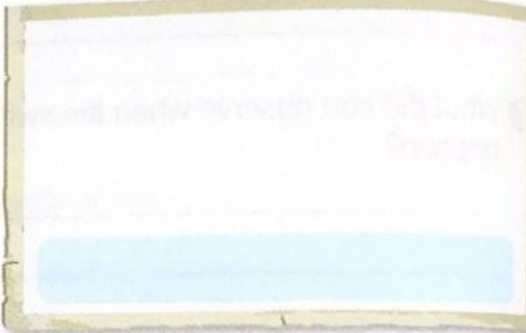

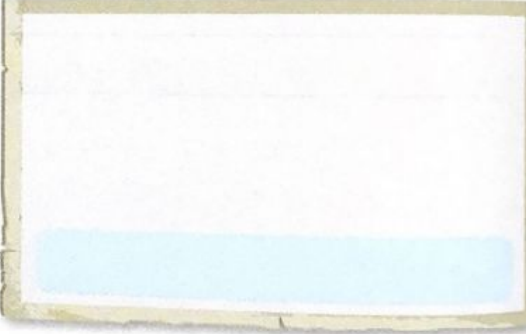




## Activity 6

### Circuit drawings

- 1 Draw the symbols for each component. Write the name of each symbol.

Component	Symbol
(a) 	
(b) 	
(c) 	



Component

Symbol


(d)



(e)

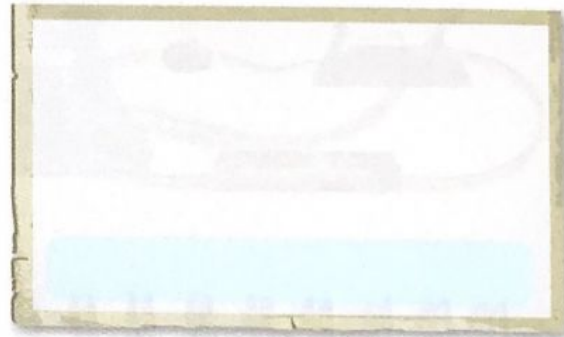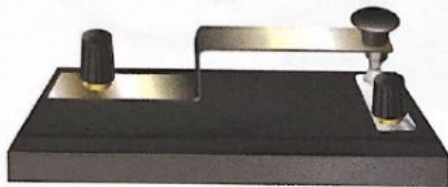

(f)

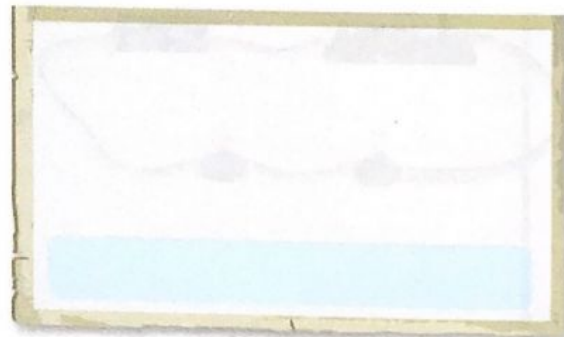

(g)

