

2 Draw lines to connect the circuit to the correct circuit diagram.

