

circuit diagrams

Focus

- 1 Draw lines linking each component with its symbol.

